

EE214: A Signal Processing Chain

Madhav Desai

April 3, 2019

A typical real-time system

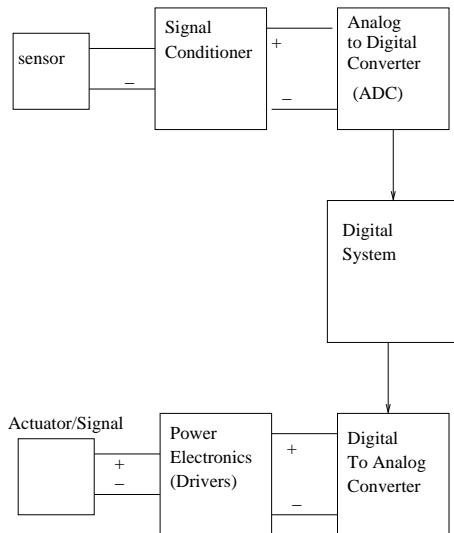


Figure: Real-time system

A 3-bit ADC

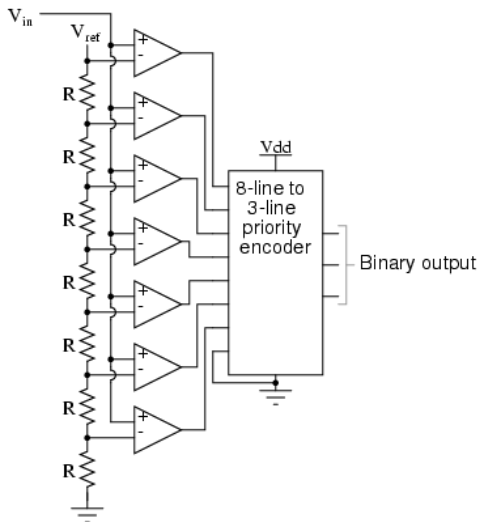


Figure: A Flash ADC (figure taken from <https://www.allaboutcircuits.com/textbook/digital/chpt-13/flash-adc/>)

A successive approximation 8-bit ADC

```
int result[] = {0,0,0,0,0,0,0,0};  
void convertToDigital (float x) {  
    int i;  
    for(i=7; i >= 0; i--)  
    {  
        if (x < epsilon)  
            break;  
        if(x > 0.5) {  
            result[i] = 1;  
            x = 2*(x-0.5);  
        }  
        else {  
            result[i] = 0;  
            x = 2*x;  
        }  
    }  
}
```

Interface to a successive approximation ADC

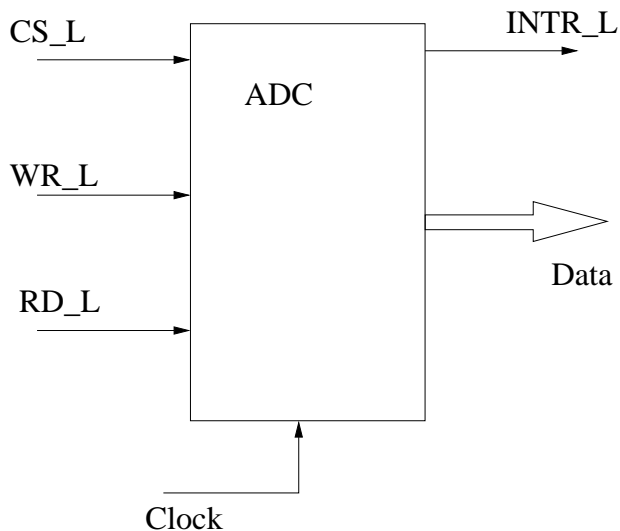


Figure: ADC Interface

Algorithm to Interface to a successive approximation ADC

Initially, $CS_L = WR_L = RD_L = 1$.

1. Make $CS_L = 0$. This initializes the ADC.
2. Make $WR_L = 0$. This starts conversion. Keep WR_L low for enough time.
3. Wait until $INTR_L$ becomes low. This indicates completion of conversion.
4. Make $WR_L = 1$.
5. Make $RD_L = 0$. Wait for some time. Sample Data from ADC into local register.
6. Make $RD_L = 1$.
7. Make $CS_L = 1$.
8. Go to the beginning, and repeat as per your requirement.

Read the document

The ADC-DAC interface document is available on Moodle. READ IT.

Assignment

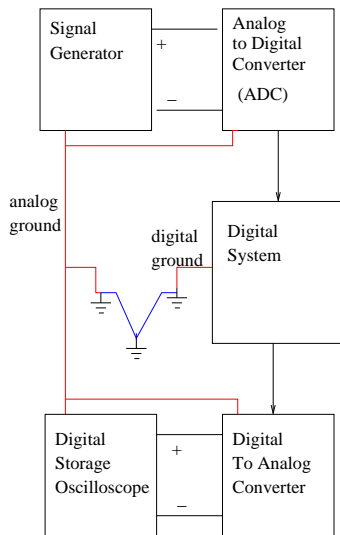


Figure: Experiment setup: use the Krypton kit for the digital system, ADC-DAC board for the rest

Assignment (part a): What you need to do

- ▶ You are given a specified sampling frequency, for example 1KHz.
- ▶ Design a circuit which will sample an analog signal at the sampling frequency (in this case, once every millisecond).
- ▶ The circuit should interface to the ADC and should implement the interface algorithm consistent with the ADC interface.
- ▶ The output of the circuit should be fed to the DAC.
- ▶ Observe inputs and outputs for various applied sinusoidal inputs (frequencies up to 500Hz in this case). Amplitudes should be varied within safe limits.

Assignment (part a): Hints

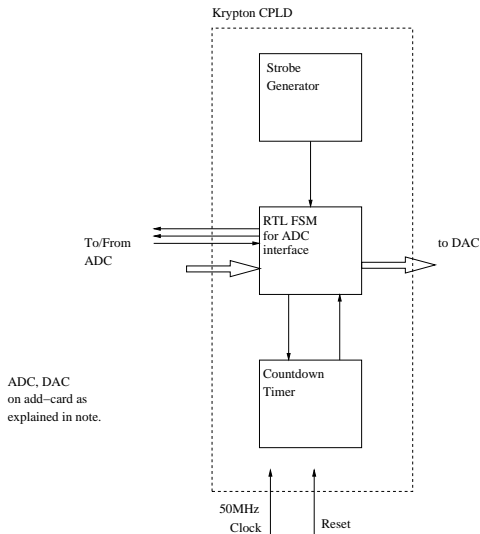


Figure: Recommendation: try to break your system into smaller subsystems.

Assignment (part b)

Let $x(k)$ be the k^{th} sample generated from the ADC. We design a digital system with output $y(k)$ which computes

$$y(k) = \frac{\sum_{m=0}^8 x(k-m)}{8}$$

This is called a moving-average filter, and can be rewritten as

$$y(k) = y(k-1) + \frac{x(k) - x(k-8)}{8}$$

You are required to implement such a digital filter to process the ADC samples and drive the result to the DAC.

Assignment (part b): hints

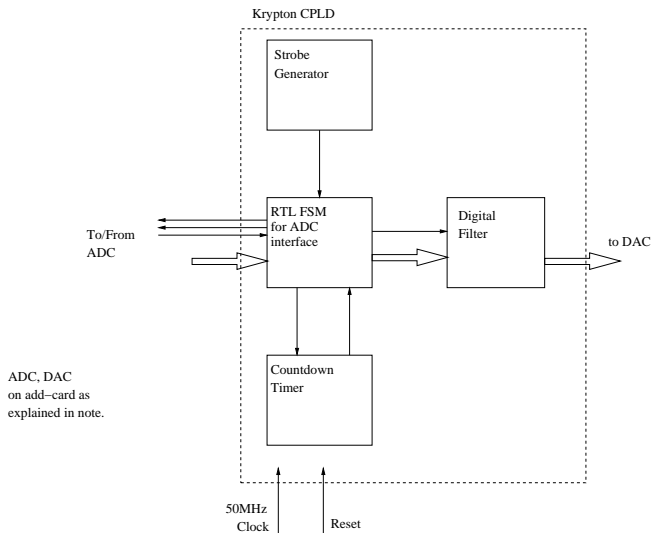


Figure: Recommendation: Incorporating the digital filter into your design

Assignment (part b): measurements

You will measure the frequency response of this filter.

- ▶ Fix the amplitude of the input signal to the ADC (say 5V peak-to-peak).
- ▶ Vary the frequency of the input signal from 50Hz to 500Hz in steps of 50Hz. For each frequency, measure the amplitude of the output signal (out of the DAC).
- ▶ Plot the ratio of amplitudes (output/input) as a function of frequency.
- ▶ What do you observe from this plot?

Winding up

Final exam will be 13 April 2019. You can submit your work for this assignment by April 30.