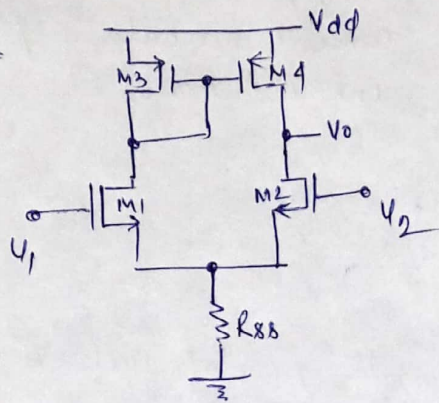


# Quiz-1 - EE-204

Ques.



M1 & M2 are matched

$$g_{m1} = g_{m2} = g_m$$

$$r_{o1} = r_{o2} = r_o$$



Similarly M3 & M4 are matched

$$g_{m3} = g_{m4} = g_m$$

$$r_{o3} = r_{o4} = r_o$$

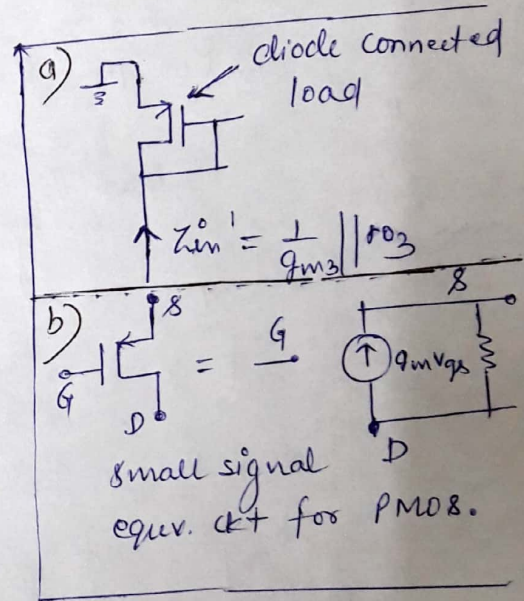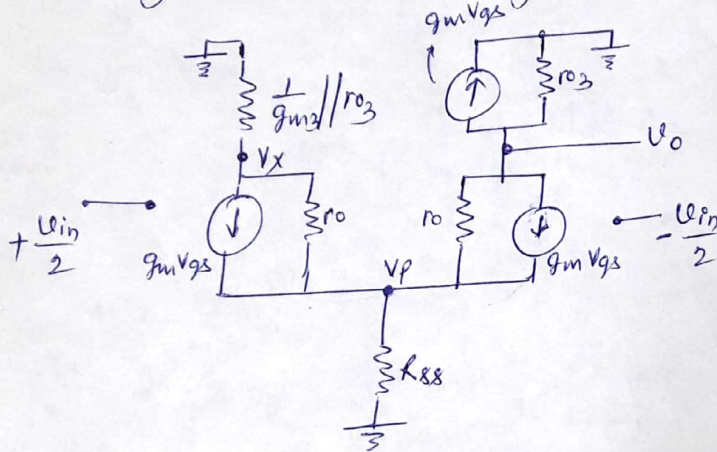Part (a) Calculating  $A_{DM} = \frac{V_o}{U_1 - U_2} = \frac{V_o}{U_{in}}$

Since  $\lambda \neq 0$ , so we need to write KCL ~~and~~ at every node for finding  $A_{DM}$ .



Writing KCL @ node  $V_p$

$$\Rightarrow \frac{V_p - V_x}{r_o} + \frac{V_p - V_o}{r_o} + \frac{V_p}{R_{ss}} = g_m \left( \frac{U_{in}}{2} - V_p \right) + g_m \left( -\frac{U_{in}}{2} - V_p \right)$$

$$V_p \left[ \frac{2}{r_o} + \frac{1}{R_{ss}} + 2g_m \right] = \frac{V_x + V_o}{r_o}$$

$$\frac{V_p}{R_{ss}} = \frac{(V_x + V_o)}{[2R_{ss} + r_o + 2r_o R_{ss} g_m]}$$


$\Rightarrow$  this expression will give the amount of current flowing into  $R_{ss}$ . i.e.  $\left( \frac{V_p}{R_{ss}} \right)$

$\frac{(V_x + V_o)}{2R_{ss} + r_o + 2r_o R_{ss} g_m}$  Very small quantity (in few tens of millivolts)  $\approx 0$

very large quantity (in orders of Mega)

Hence, there is no current flowing into  $R_{ss}$ . ~~Here~~ So, we can consider node  $V_p = 0$ .

in differential mode

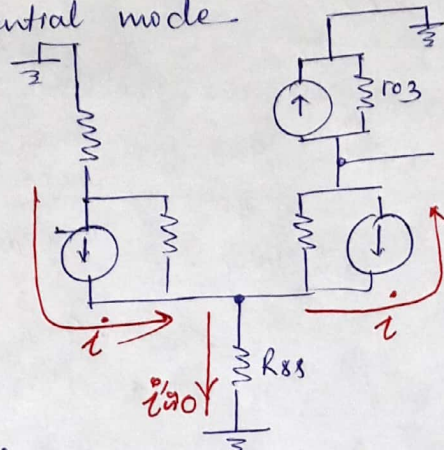

This fig. is to show how current avoids to flow into  $R_{ss}$  branch.

Now, since  $V_p = 0$ , we can write KCL at node  $V_x$  &  $V_o$ .

$$\frac{V_x}{r_o} + g_m \frac{V_{in}}{2} + \frac{V_x}{\frac{1}{g_{m3}} \parallel r_{o3}} = 0$$

$$\frac{V_x}{r_o} + g_m \frac{V_{in}}{2} + V_x g_{m3} = 0$$

$\star \frac{1}{g_{m3}} \parallel r_{o3} \approx \frac{1}{g_{m3}}$   
 $\star$  generally,  $\frac{1}{g_{m3}}$  is much lower than  $r_{o3}$

$$V_x = \frac{-g_m V_{in} / 2}{\left[ \frac{1}{r_o} + g_{m3} \right]} \quad \text{--- (1)}$$

KCL @ node  $V_o$

$$\frac{V_o}{r_o} + g_m \left( -\frac{V_{in}}{2} \right) + g_m V_x + \frac{V_o}{r_{o3}} = 0$$

$$V_o \left[ \frac{1}{r_o} + \frac{1}{r_{o3}} \right] = g_m \frac{V_{in}}{2} - g_{m3} V_x \quad \text{--- (2)}$$

putting value of eqn (1) into (2) and simplification.

$$\frac{V_o}{V_{in}} = \frac{g_m}{2} \frac{[1 + 2r_o g_{m3}]}{[1 + r_o g_{m3}]} (r_o \parallel r_{o3})$$



Part (b) Calculate  $A_{cm} = \frac{V_o}{V_c}$

In this case, since common i/p  $V_c$  is applied, so the current would definitely go into  $R_{ss}$ . Hence,  $V_p$  cannot be considered zero.

applying KCL @ node  $V_x$ .

$$\Rightarrow V_x g_{m3} + \frac{V_x - V_p}{r_o} + g_m (V_c - V_p) = 0 \quad \text{--- (1)}$$

applying KCL @ node Vp.

$$\Rightarrow \frac{V_p}{R_{SS}} + \frac{V_p - V_x}{r_o} + \frac{V_p - V_o}{r_o} = 2g_m(V_o - V_p) \quad \text{--- (2)}$$

applying KCL @ node  $V_0$

$$\Rightarrow \frac{V_o - V_f}{r_{o2}} + g_m(V_c - V_f) + \frac{V_o}{r_{o3}} + g_{m3}V_x = 0 \quad \text{--- (3)}$$

putting  $\frac{V_x - V_p}{r_o}$  from (1) and  $\frac{V_o - V_p}{r_o}$  from (3) into eqn (2),

We get, after simplification

$$\Rightarrow V_p = -2V_x g_{m3} R_{ss} - \frac{V_o R_{ss}}{r_{o3}} \quad \text{--- (4)}$$

subtracting eqn (2) from eqn (1), we get

$$V_x = \frac{V_o r_o}{r_o || r_{o3}} \quad \text{--- (5)}$$

simplifying eqn (1),

$$V_X \left( g_{m3} + \frac{1}{r_o} \right) + V_P \left( -g_m - \frac{1}{r_o} \right) = -g_m V_C$$

$$g_m V_c = V_p \left( \frac{1}{r_o} + g_m \right) - V_x \left( g_{m3} + \frac{1}{r_o} \right)$$

$$g_m V_c = V_p g_m - V_x \left( g_{m3} + \frac{1}{r_o} \right) - \textcircled{6} \left[ \frac{1}{r_o} + g_m \parallel g_m \right]$$

putting the values of  $v_x$  &  $v_y$  from eqn (5) & (4) into eq (6). we get

$$\frac{V_o}{V_c} = \frac{-g_m(r_o \parallel r_{o3})}{(g_{m3}r_o + 1) + \frac{R_{S3}g_m(r_o \parallel r_{o3})}{r_{o3}} + 2g_mg_{m3}R_{S3}r_o}$$

