


EE 204-2018-2 Analog Circuits

Homework #5 Solution

Question 1:

Q1 Solution

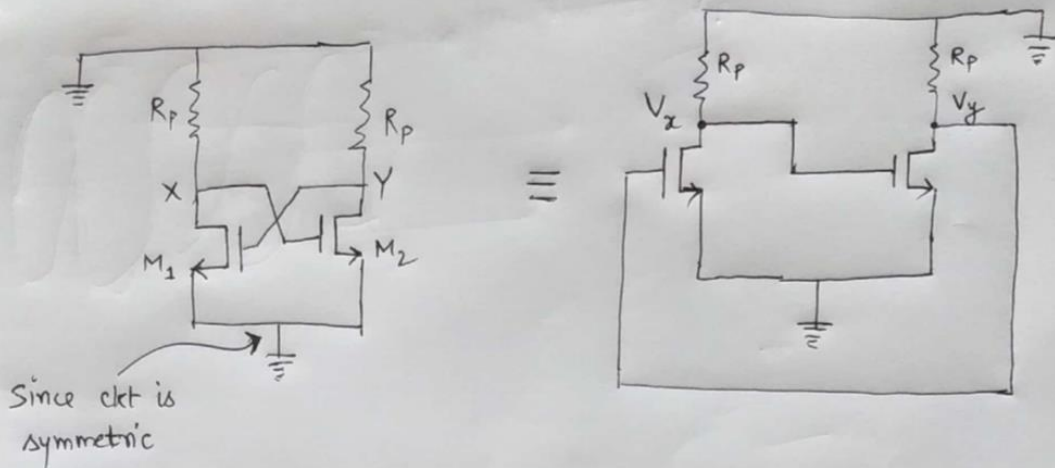(i) At oscillation C_p & L_p cancel each other out. Hence the eqv. ckt. is:



* Assuming $\lambda = 0$

$$\text{Loop gain} = \text{Gain}_{\text{First stage}} \times \text{Gain}_{\text{Second stage}}$$

$$= (-g_{m1} R_p) \times (-g_{m2} R_p)$$

$$\text{Loop Gain} = g_{m1} g_{m2} R_p^2 \equiv g_m^2 R_p^2 \quad (\text{if } g_{m1} = g_{m2} = g_m)$$


Applying the Barkhausen criteria,

$$g_m^2 R_p^2 > 1 \Rightarrow 2\mu_n C_{ox} \frac{W}{L} I_D R_p^2 > 1$$

Where $I_D = \frac{I_{SS}}{2}$, Hence

$$I_{SS}|_{\min} = \frac{1}{\mu_n C_{ox} \frac{W}{L} R_p^2}$$

(ii)

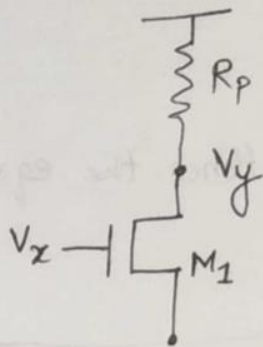

$$V_{DS} > V_{GS} - V_{Th}$$

$$V_y > V_x - V_{Th}$$

$$V_y - V_x > -V_{Th}$$

Similarly from M_2 we get

$$V_x - V_y > -V_{Th}$$

i.e. $-V_{Th} < V_y - V_x < V_{Th}$

Max diff of $V_y - V_x$ is $I_{ss} R_p$ hence


$$I_{ss} R_p < V_{Th}$$

$$I_{ss}|_{\max} = \frac{V_{Th}}{R_p}$$


Question 2:

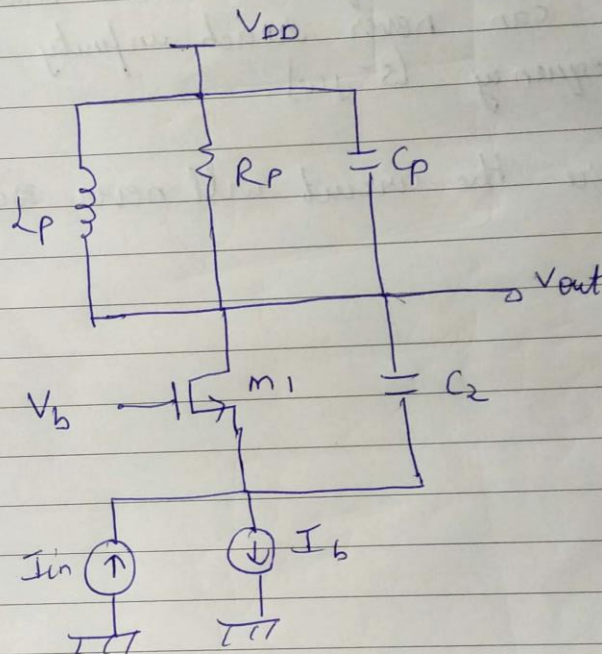Question 2

To obtain the closed-loop gain, the following circuit is analysed:-



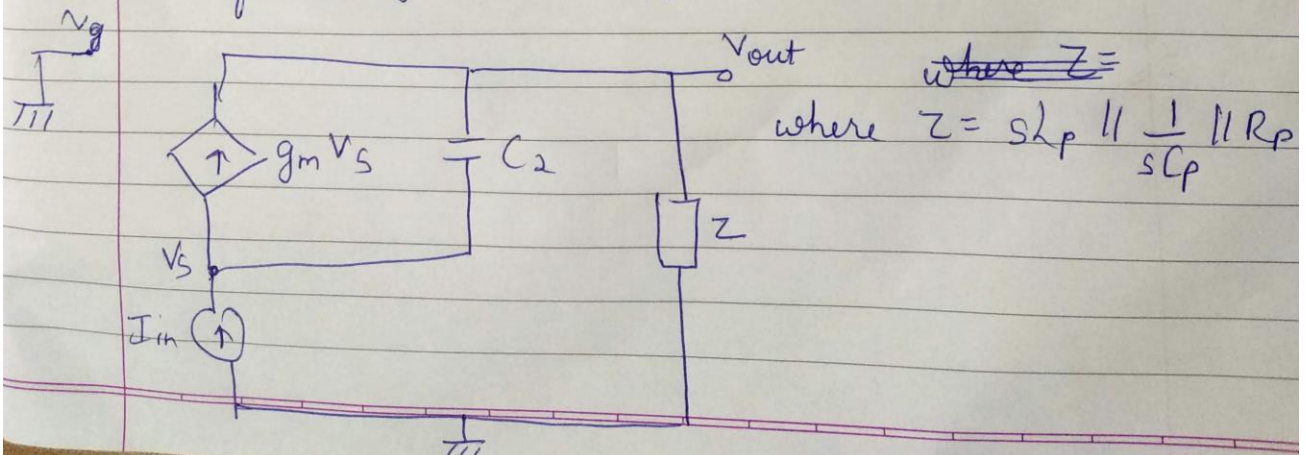In the above case, I_{in} is the input current. To obtain the gain, V_b and V_{DD} are grounded whereas I_b is opened. We have the following small signal circuit




From the above figure we find -

$$\frac{V_{out}}{I_{in}} = Z = sL_p \parallel \frac{1}{sC_p} \parallel R_p$$

From the above equation we see that the gain can never reach infinity at any frequency ($s = j\omega$).

Therefore the circuit will never oscillate.

Question 3:

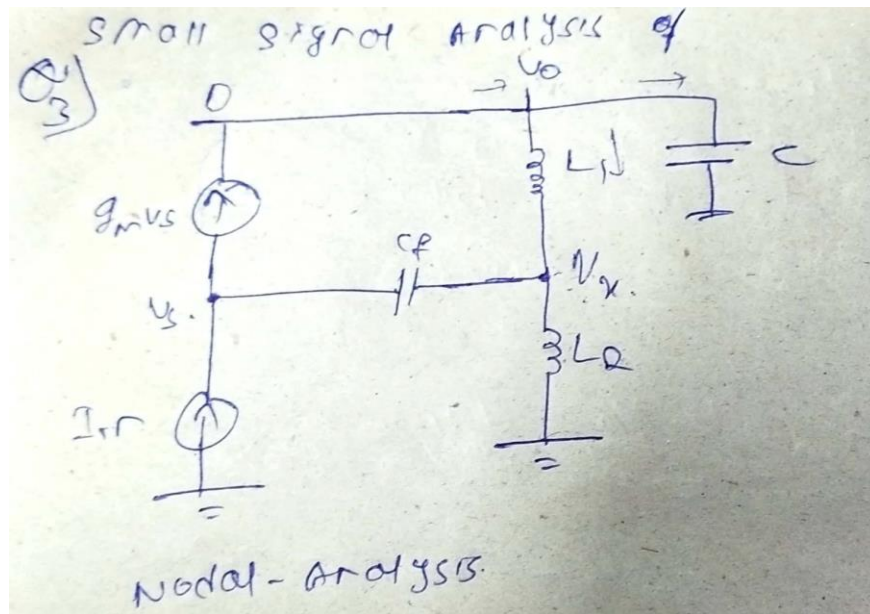

$$\frac{V_0 - V_x}{sL_1} + V_0 sC - g_m V_s = 0 \quad \text{--- (1)}$$

$$I_{in} = g_m V_s + \frac{(V_s - V_x) s C_f}{sL_1} \quad \text{--- (2)}$$

$$\frac{V_x}{sL_2} + (V_x - V_s) s C_f + \left(\frac{V_x - V_0}{sL_1} \right) = 0 \quad \text{--- (3)}$$

~~(1)~~ (2)
$$I_{in} = g_m V_s + s C_f V_s - s V_x C_f$$

$$I_{in} = V_s (g_m + s C_f) - s V_x C_f$$

$$V_s = \frac{I_{in} + s V_x C_f}{g_m + s C_f} \quad \text{--- (4)}$$

$$\frac{V_o - V_x}{sL_1} + V_o sC + g_m V_s = 0$$

$$\frac{V_o - V_x}{sL_1} + V_o sC - g_m \left(\frac{I_{in} + sV_x C_f}{g_m + sC_f} \right) = 0$$

$$\frac{V_o + V_o sC}{sL_1} - \frac{V_x}{sL_1} - \frac{g_m I_{in}}{g_m + sC_f} - \frac{g_m sV_x C_f}{g_m + sC_f} = 0$$

$$\frac{V_o}{sL_1} + V_o sC - \frac{g_m I_{in}}{g_m + sC_f} = V_x \left\{ \frac{1}{sL_1} + \frac{g_m sC_f}{g_m + sC_f} \right\}$$

$$\frac{\left\{ \frac{V_o}{sL_1} + V_o sC - \frac{g_m I_{in}}{g_m + sC_f} \right\}}{\frac{1}{sL_1} + \frac{g_m sC_f}{g_m + sC_f}} = V_x \quad \text{--- (5)}$$

from eq. 4

$$V_s = \frac{I_{in}}{g_m + sC_f} + \frac{sC_f}{g_m + sC_f} \left\{ \frac{V_o}{sL_1} + V_o sC - \frac{g_m I_{in}}{g_m + sC_f} \right\}$$

$$V_s = \frac{I_{in}}{g_m + sC_f} + \frac{sC_f}{g_m + sC_f} \left\{ \frac{V_o(g_m + sC_f)}{sL_1} + \frac{V_o s^2 L_1 C - g_m I_{in} sL_1}{sL_1} \right\}$$

$$g_m + sC_f + g_m sC_f$$

--- (6)

$$\rightarrow V_o \left(\frac{1}{sL_1} + sC \right) - \frac{V_u}{sL_1} - g_m V_s = 0$$

$$\rightarrow V_o \left(\frac{1}{sL_1} + sC \right) - \frac{1}{sL_1} \left\{ \frac{V_o}{sL_1} + V_o sC - \frac{g_m I_{in}}{g_m + sC_f} \right\}$$

$$\frac{1 + \frac{g_m sC_f}{g_m + sC_f}}{sL_1}$$

$$- g_m \left\{ \frac{I_{in}}{g_m + sC_f} + \frac{sC_f}{g_m + sC_f} \left\{ \frac{V_o (g_m + sC_f)}{+ V_o s^2 L_1 C - g_m I_{in} s L_1} \right\} \right\}$$

$$\frac{g_m + sC_f + g_m sC_f}{g_m + sC_f}$$

$$\rightarrow V_o \left(\frac{1}{sL_1} + sC \right) + V_o \left\{ \frac{-1}{s^2 L_1} + sC \right\}$$

$$\frac{\frac{1}{sL_1} + \frac{g_m sC_f}{g_m + sC_f}}{g_m + sC_f}$$

$$+ I_{in} \left\{ - \frac{g_m}{g_m + sC_f} \right\}$$

$$\frac{\frac{1}{sL_1} + \frac{g_m sC_f}{g_m + sC_f}}{g_m + sC_f}$$

$$- g_m \left\{ \frac{I_{in}}{g_m + sC_f} + \frac{sC_f}{g_m + sC_f} \left\{ \frac{V_o (g_m + sC_f) + V_o s^2 L_1 C}{- g_m I_{in} s L_1} \right\} \right\}$$

$$\frac{g_m + sC_f + g_m sC_f}{g_m + sC_f}$$

Solve for $\frac{V_o}{I_{in}}$ from above equation and equate I_o and gives the condition for frequency of oscillations.