
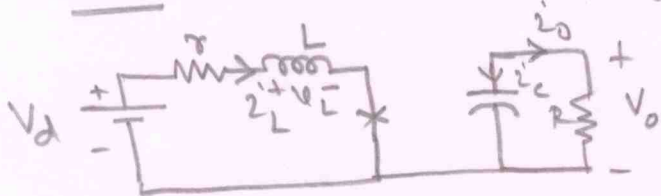


Q1


When S is on

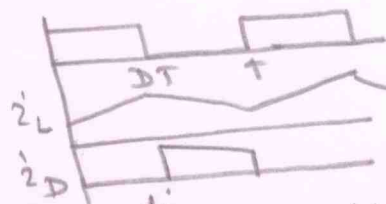

$$V_L = L \frac{di_L}{dt} = V_d - r i_L$$



When S is off

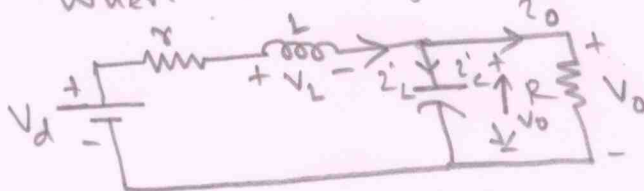

$$V_L = L \frac{di_L}{dt} = V_d - V_o - r i_L$$

At steady state average voltage drop across the inductor is zero

$$\therefore (V_d - r i_L) DT + (V_d - V_o - r i_L)(1-D)T = 0$$

$$\text{or, } V_o(D-1) = r i_L - V_d$$

$$\approx r \bar{i}_L - V_d$$

$$\therefore I_o = (1-D) \bar{i}_L$$

$$\therefore \bar{i}_L = \frac{I_o}{1-D}$$

$$\approx r \frac{I_o}{(1-D)} - V_d = \frac{r}{R} \frac{V_o}{1-D} - V_d$$

$$\text{or, } V_o(1-D) = V_d - \frac{r}{R} \frac{V_o}{1-D} \quad \text{or } V_o = \frac{V_d(1-D)}{\frac{r}{R} + (1-D)^2}$$


$$\therefore \text{At } D=0, V_o = \frac{V_d}{\frac{r}{R} + 1} \times R \approx V_d \text{ (if } r \text{ is small)}$$

At  $D=1$ ,  $V_o=0$ , Hence  $V_o(\text{max})$  occurs in the range of  $0 \leq D \leq 1$

$$\frac{dV_o}{dD} = 0 \Rightarrow -\left\{ \frac{r}{R} + (1-D)^2 \right\} V_d - V_d(1-D)(2D-2) = 0$$

$$\text{or, } D = 1 - \sqrt{\frac{r}{R}}$$
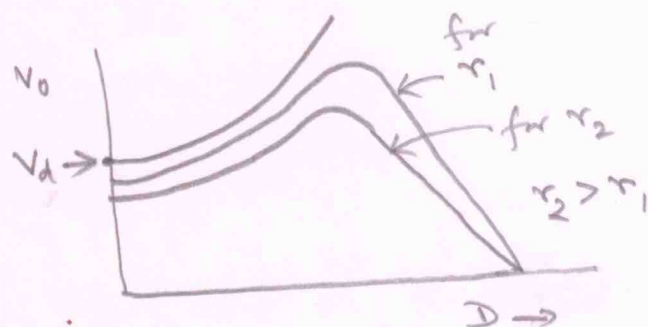
$$\therefore V_o(\text{max}) = \frac{V_{dc}}{2} \sqrt{\frac{R}{3r}}$$




82. i)  $T = 5 \times 10^{-5} \text{ s}$

$$I_{Lp} = \frac{100}{L} DT$$

and,

$$I_{Lp} - \frac{400}{L} (1-D)T = 0$$
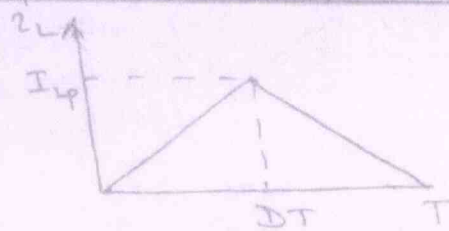
$$\therefore, \frac{100}{L} DT - \frac{400}{L} (1-D)T = 0 \therefore D = 0.8$$




ii) As  $D = 0.5$  which is less than  $0.8$ , the system operates in discontinuous mode of operation

$$\text{Power transferred} = \frac{\text{Energy stored in the inductor at } DT}{T}$$

$$I_{Lp} = \frac{100}{L} DT$$

$$= \frac{100}{100 \times 10^{-6}} \times 0.5 \times 5 \times 10^{-5}$$

$$= 25 \text{ A}$$


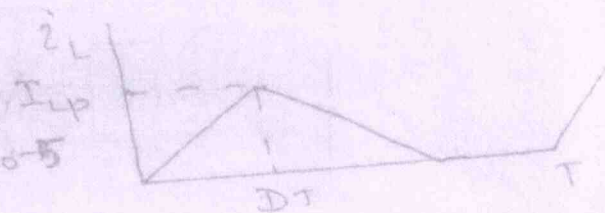


$$\therefore \text{Energy stored in the inductor at } DT = \frac{1}{2} \times L \times (25)^2 \text{ W-s}$$

$$\therefore \text{Power transferred} = \frac{1}{2} \times 100 \times 10^{-6} \times 625 \times \frac{1}{5 \times 10^{-5}} \text{ W}$$

$$= 625 \text{ Watt}$$

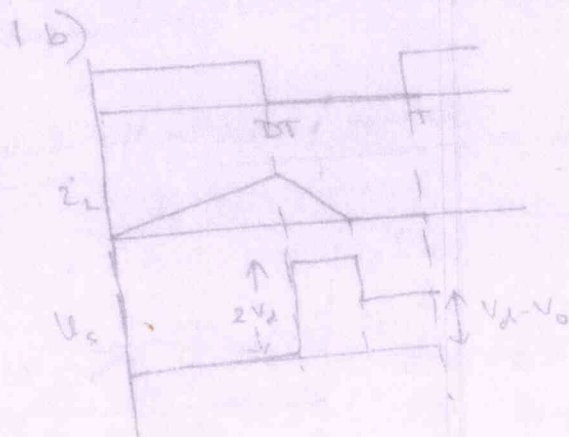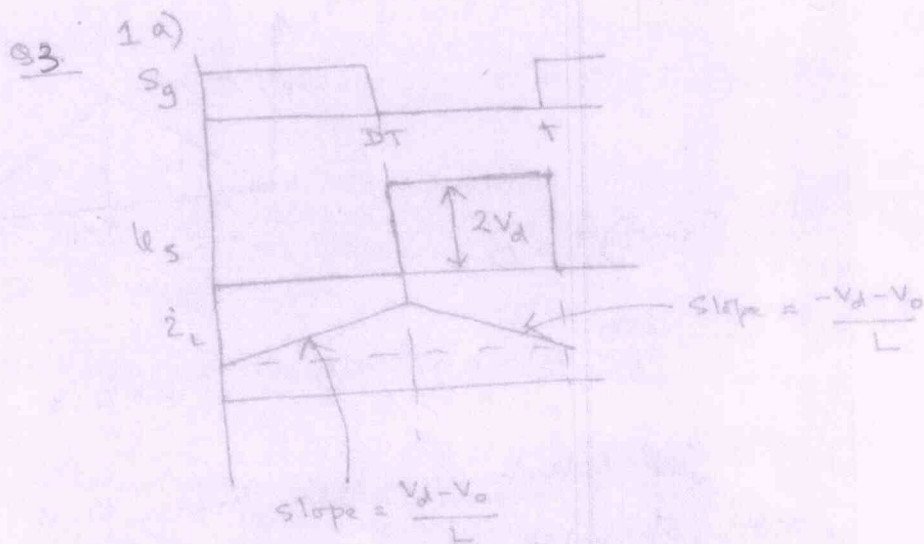iii) Inductor current will continually build up and steady state will never be reached.




2) Average voltage across the inductor is zero.

$$\therefore (V_d - V_o)DT - (V_o + V_d)(1-D)T = 0$$

$$\therefore V_o = (2D-1)V_d$$

$$I_{rr} = \frac{V_d - V_o}{L} DT = 2V_d(1-D) \frac{DT}{L}$$

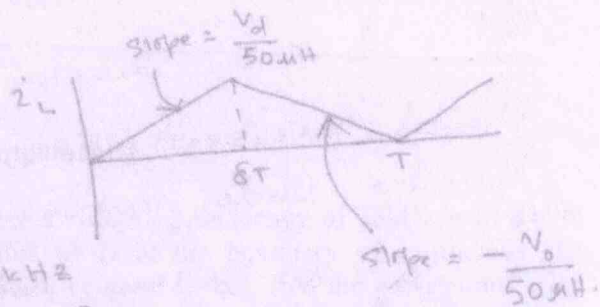Q4 As the system is on the boundary of Cont and discont. mode.



$$\frac{V_o}{V_d} = \frac{\delta}{1-\delta} \quad f = 50 \text{ kHz} \quad \therefore T = 2 \times 10^{-5} \text{ s}$$

Average load current at this condition:

$$\frac{1}{2} \frac{V_d \delta T}{50 \times 10^{-6}} \times T \times \frac{1}{T} = \frac{10}{R_L}$$

$$\text{or, } \frac{1}{2} \cdot \frac{(1-\delta)}{\delta} 10 \times \frac{1}{50 \times 10^{-6}} \times \cancel{\delta} \times 2 \times 10^{-5} = \frac{10}{R_L}$$

$$\text{or, } (1-\delta) \frac{5}{5 \times 10^{-5}} \times 2 \times 10^{-5} = \frac{10}{R_L}$$

$$\text{or, } 2(1-\delta) = \frac{10}{R_L}$$

$$\text{or, } 1-\delta = \frac{5}{R_L} \quad \text{or, } \delta = 1 - \frac{5}{R_L}$$

$$\therefore V_d = \frac{10(1-\delta)}{\delta} = \frac{10 \cdot \frac{5}{R_L}}{\frac{R_L-5}{R_L}} = \frac{50}{R_L-5}$$

$$\begin{aligned} I_{D(\text{peak})} &= \frac{V_d \delta T}{50 \times 10^{-6}} \\ &= \frac{50}{(50 \times 10^{-6})(R_L-5)} \times 0.5 \times 2 \times 10^{-5} \text{ A} \\ &= \frac{10}{R_L-5} \text{ A} \end{aligned}$$


Q5  $\delta = 0.5$ , therefore the o/p voltage should have been 50V, if the converter operates under continuous mode of conduction.

As  $V_o = 80 > 50V$ , the converter is operating under discontinuous mode of conduction.

$$I_{Lp} = \frac{20}{2.5 \times 10^{-3}} T \times 0.5 \quad S_g$$

$$T = \frac{1}{5 \times 10^3}$$

$$= 2 \times 10^{-4}$$

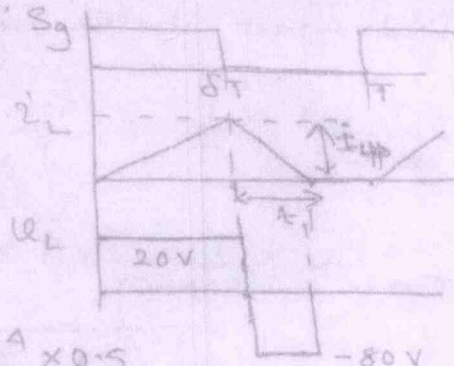

$$\therefore I_{Lp} = \frac{20}{2.5 \times 10^{-3}} \times 2 \times 10^{-4} \times 0.5$$

$$= 0.8A$$

Average voltage drop across the inductor is zero.

$$\therefore 20 \times 1 \times 10^{-4} - 80 t_1 = 0$$

$$\therefore t_1 = \frac{20 \times 10^{-4}}{80} = 0.25 \times 10^{-4}$$

$$\therefore \bar{i}_L = I_o = \frac{1}{2} \times (1.25 \times 10^{-4}) \times 0.8 \times \frac{1}{2 \times 10^{-4}}$$

$$= 0.25A$$

$$\therefore R_L = \frac{80}{0.25} \Omega = 320 \Omega$$