

# Design of MOSFET Differential Amplifiers

**Wadhwani Electronics Lab**

Department of Electrical Engineering  
Indian Institute of Technology Bombay  
Jan 2019

- \* In this experiment, we wish to design and test Simple Current Mirror.
- \* We will also design and test MOSFET Differential Amplifiers with resistive and active loads.(Using ALD1106 and ALD1107).
- \* This experiment mainly aims at understanding the internal working of OPAMP.

- 1 Read up on differential amplifiers. Familiarize yourself with the terms "Common Mode Gain" and common mode rejection ratio (CMRR).
- 2 Design the circuits to be used in each of the three parts of the experiment.
- 3 Draw the small signal model of differential amplifier with active load.
- 4 All the tasks listed under Pre Lab work must be included in your post lab report.
- 5 **Simulate all your designs in NGSPICE for better understanding.**

# Simple Current Mirror

Current sources are extensively designed and used to bias different kinds of circuits. An ideal current source supplies a constant current irrespective of the voltage supplied across it. In this experiment, we study following current source which is designed using MOSFETs.

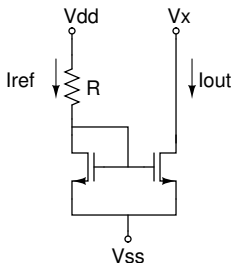


Figure: 1

$$I_{ref} = \frac{V_{DD} - V_{GS}}{R}$$

If sizes( $W/L$ ) of both transistors are equal(They are indeed equal in ALD1106 IC), then same current  $I_{ref}$  is replicated to  $I_{out}$ . Therefore,  $I_{out} = I_{ref}$

# Differential amplifier with resistive load

Figure 2 shows a Differential Amplifier which you have already studied in class. Analyze the circuit and find the expression for differential as well as common-mode gain. Write the derivation in postlab report.

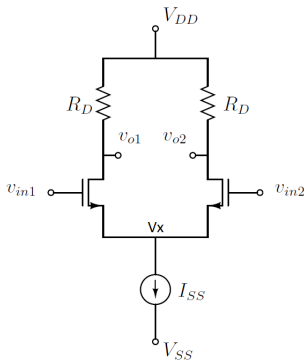


Figure: 2

# Theory and Design Procedure

Small signal model of the above circuit is as follows :

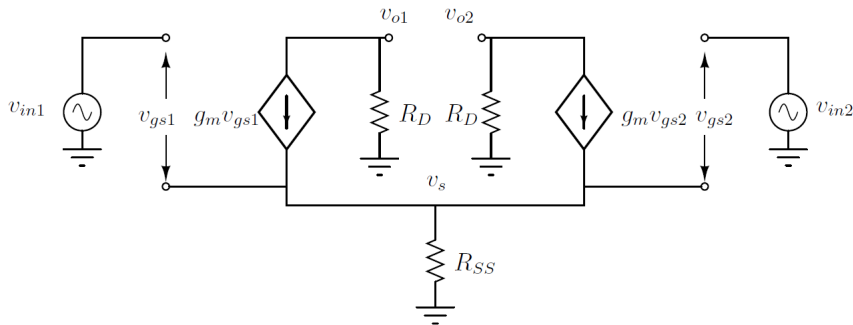


Figure 3: Small signal model of MOS Differential Amplifier

# Part 1- Simple MOSFET Differential Amplifier

In this part, we will use the same circuit as shown in Figure 2. Instead of current source, use current mirror as given in Figure 1 (Precaution: Set the supply voltages properly before connecting them to the circuit. The maximum supply the device can tolerate is roughly  $-5.5V - 5.5V$ )

- 1 Assemble the circuit, to get  $I_{out}$  of 1mA. Calculate the value of  $K_n$  or  $K_p$  with the help of the values tabulated in the datasheet.
- 2 For supply voltages  $V_{DD} = 4.5V$  and  $V_{SS} = -4.5V$ , find the value of  $R_D$  required for a gain of 7. Will the output voltage swing be symmetric?
- 3 Wire up your circuit and apply a 50 mV peak, 1 kHz sine wave to (i)  $v_{in1}$  and (ii)  $v_{in2}$ . While applying a signal to one input, keep the other input grounded. Ensure that there is no distortion in the output. Measure the differential voltage gain  $A_d$  in each case. (How will you observe differential signals on the DSO?)
- 4 Find out the maximum symmetrical output swing of your circuit at 1 kHz.

# Part 1 - Simple MOSFET Differential Amplifier

- 5 Repeat step 3 for frequencies 10 kHz, 100 kHz and 500 kHz and 1 MHz.
- 6 Now short both the input terminals and apply a common-mode signal. Measure the common-mode voltage gain  $A_c$  at the above frequencies. Calculate the CMRR (in dB) for each frequency.
- 7 Measure the input offset voltage of your differential amplifier (you may neglect the effects of input bias current).
- 8 Compare your results (differential gain, CMRR, offset voltage) with two other groups and tabulate them.



## Part 2 - Differential Amplifier with Active Load

We will now replace the two drain resistors  $R_D$  in Figure 2 by a PMOS current mirror, as in Figure 4, and take a single-ended output.

Why do we use this configuration over resistive load? Mention reasons in postlab report.

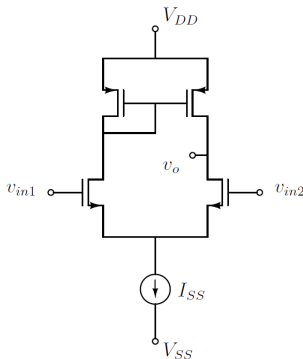


Figure 4: Differential Amplifier with Active Load

## Part 2 - Differential Amplifier with Active Load

- 1 Use supply voltages  $V_{DD} = 4.5V$  and  $V_{SS} = -4.5V$ , find the expression for gain, find the value of  $I_{SS}$  required for a gain of 50. (Hint: This time, the drain-source resistance  $r_o$  of the transistors need to be considered. Given the channel length modulation parameter  $\lambda$  for the NMOS and PMOS are approximately 0.036).
- 2 Use an appropriately designed current mirror for  $I_{SS}$ . (Keep the value of  $I_{SS}$  less than 100 $\mu$ A).
- 3 You may have to vary the potentiometer in current mirror to adjust the  $I_{SS}$  which in turn adjusts the gain of the amplifier.
- 4 Wire up your circuit and apply a 20 mV peak, 1 kHz sine wave to (i)  $v_{in1}$  and (ii)  $v_{in2}$ . Measure  $A_d$  in each case.

## Part 2 - Differential Amplifier with Active Load

- 5 Report the dependence of Gain on  $I_{SS}$ . Mention all the challenges you face in designing and explain why?.
- 6 Find out the maximum symmetrical output swing of your circuit at 1 kHz.
- 7 Repeat step 3 for frequencies 10 kHz, 100 kHz and 500 kHz and 1 MHz.
- 8 Measure the common-mode voltage gain  $A_c$  and the CMRR (in dB) at the above frequencies.
- 9 Measure the input offset voltage of your differential amplifier.
- 10 Compare your results with two other groups and tabulate them.