

Assignment-2	EE204 - Analog Circuits	4 th Feb 2019
Submission Deadline-17.00 11th Feb, 2019	Submission Protocol: Notebook submission	Comment: Partial

1.A	<p>Consider the differential amplifier we have discussed in the class with the following parameters: $g_{m1} = g_{m2} = 2 \text{ mS}$, $R_{D1} = R_{D2} = 20 \text{ k}\Omega$, $R_{SS} = 200 \text{ k}\Omega$, $r_{o1} = r_{o2} = \infty$.</p> <ol style="list-style-type: none"> Find out the differential gain (A_{DM}) of the amplifier. Find out the common mode to differential model conversion (A_{CM-DM}) when: <ol style="list-style-type: none"> $g_{m1} = g_{m0} + \Delta g_m / 2$ and $g_{m2} = g_{m0} + \Delta g_m / 2$ where $g_{m0} = 2 \text{ mS}$ and $\Delta g_m = 0.2 \text{ mS}$ and all other parameters remain same. Find out CMRR. $R_{d1} = R_{D0} + \Delta R_D / 2$ and $R_{D2} = R_{D0} + \Delta R_D / 2$ where $R_{D0} = 20 \text{ k}\Omega$ and $\Delta R_D = 2 \text{ k}\Omega$ and all other parameters remain same. Find out CMRR. Both g_m and R_d are varying as in (a) and (b). Repeat (a), (b) and (c) when $r_{o1} = r_{o2} = 50 \text{ k}\Omega$. Also find out A_{DM} and CMRR for this case. Comment on the effect of the finite output resistance of the transistors. Find out the sensitivity of the A_{CM-DM} for a mismatch of R_D and r_o. Also qualitatively explain your observations obtained from the calculations.
1.B	<p>Consider nMOS with the following characteristics: $k' = 1 \text{ mA/V}^2$, $V_T = 1 \text{ V}$, $R_D = 10 \text{ k}\Omega$, $\lambda = 0$.</p> <ol style="list-style-type: none"> Design a perfectly matched differential amplifier with multiple instances of the above nMOS for a bias current of $I_{SS} = 8 \text{ mA}$ and $R_{SS} = \infty$. Plot $V_{O1} - V_{O2}$ versus $V_{IN1} - V_{IN2}$. Plot in any software and attach the plot. Plot $I_{DS1} - I_{DS2}$ versus $V_{IN1} - V_{IN2}$. Plot in any software and attach the plot. Find out A_{DM} for the first and second harmonic differential output as a function of the small signal differential input amplitude.