
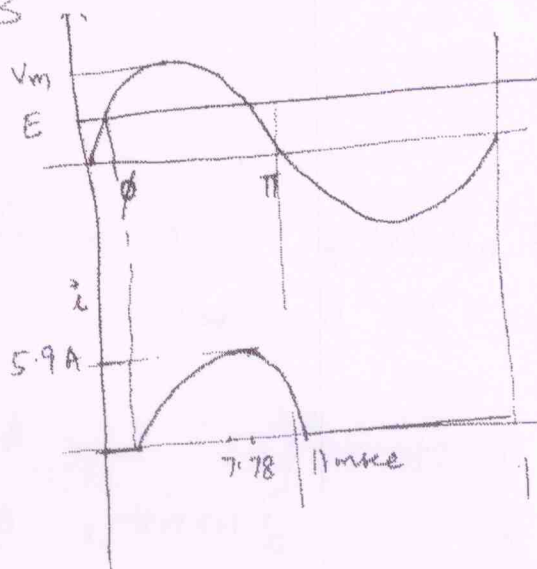


Assignment - 3

①

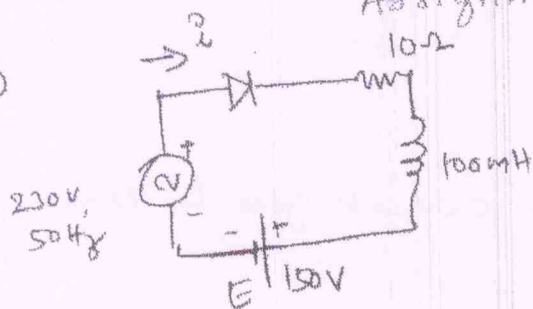

Assume that the diode starts conducting at $\omega t = \phi$ & conducts till the current falls to zero.

$$\phi = \sin^{-1} \left\{ \frac{E}{V_m} \right\} = \left\{ \sin^{-1} \left\{ \frac{150}{325.26} \right\} \right\} = 27.46^\circ = 0.4793 \text{ rad}$$

$$V_m \sin \omega t - E = iR + L \frac{di}{dt}$$

Solving the differential equation

$$i = \frac{V_m}{Z} \sin(\omega t - \theta) - \frac{E}{R} + A e^{-R/Lt} \quad \text{--- (1)}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = 32.769 \Omega \quad \theta = \tan^{-1} \left\{ \frac{\omega L}{R} \right\} = 72.343^\circ = 1.263 \text{ rad}$$

Substituting $\omega t = \phi$, $i = 0$, and $t = \frac{\phi}{\omega} = 1.525 \text{ msec}$ in (1)

$$A = \frac{21.96}{e^{-R/Lt}} = 25.578 \text{ ampere}$$

$$\text{So } i = 9.866 \sin(\omega t - 1.2626) - 15 + 25.578 e^{-100t} \quad \text{--- (2)}$$


differentiating (2) and eqnating to zero

$$\frac{di}{dt} = 3099 \cos(314t - 1.2626) - 2557.8 e^{-100t} = 0$$

Solving for t , I_{max} occurs at $t = 7.78 \text{ msec}$

$$I_{\text{max}} = i|_{t=7.78 \text{ msec}} = 5.9 \text{ A}$$

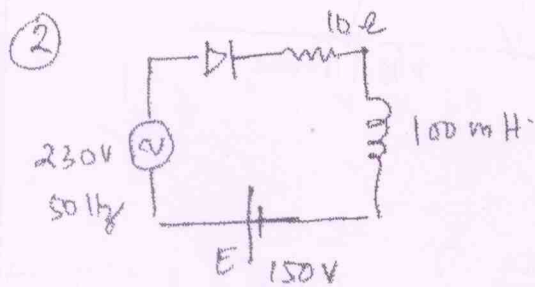Substituting $i = 0$ in (2), the current goes to zero at $t = 11 \text{ msec}$.



Assuming that the diode starts conducting at $\omega t = \phi$, where

$$\phi = \sin^{-1} \left\{ \frac{E}{V_m} \right\}$$

$$= -0.4793 \text{ radians}$$

$$i = \frac{V_m}{Z} \sin(\omega t - \theta) + \frac{E}{R} + A e^{-R/Lt} \quad \text{--- (1)}$$

At $\omega t = \phi$, $i = 0$ and $t = \frac{\phi}{\omega} = -1.525 \text{ msec}$. Substituting these values in (1),


$$A = -4.538 \text{ A}$$

$$\text{So } i = 9.866 \sin(\omega t - 1.2626) + 15 - 4.538 e^{-100t} \quad \text{--- (2)}$$

For discontinuous conduction mode, the current should go to zero before it reaches $(2\pi + \phi) = 5.804 \text{ rad}$

$$\text{But } i|_{(2\pi + \phi) = \omega t} = 4.56 \text{ A} > 0$$



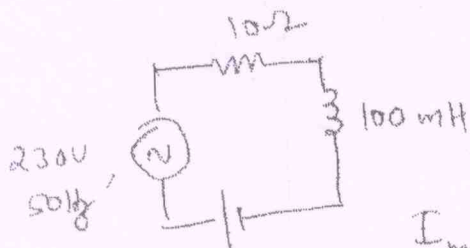
So continuous conduction mode, and the diode can be removed. In steady state



$$i = \frac{V_m}{Z} \sin(\omega t - \phi) + \frac{E}{R}$$

$$\phi = 1.2626 \text{ rad}$$
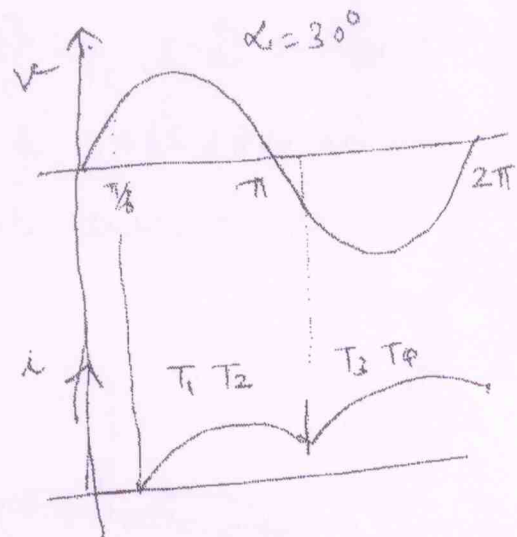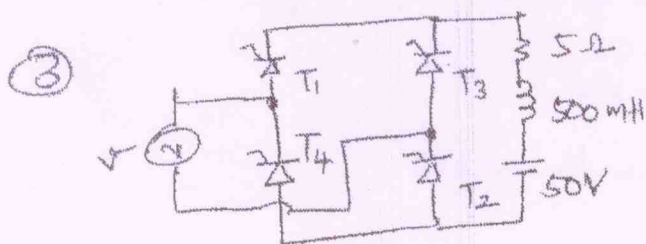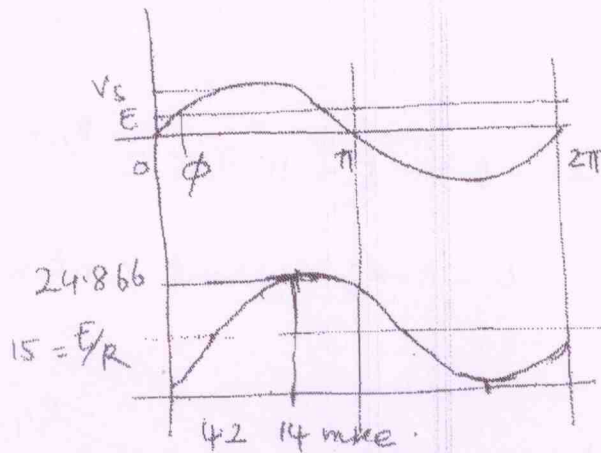
$$I_{\text{max}} = \frac{V_m}{Z} + \frac{E}{R} = 24.866 \text{ A at } \omega t = 4.404 \text{ radians}$$



$$V_m \sin \omega t = L \frac{di}{dt} + iR + E$$

$$i = \frac{V_m \sin \omega t - E}{L (D + R/L)}$$

Solving the differential eqn,

$$i = \frac{\sqrt{2} V_s}{Z} \sin(\omega t - \theta) - \frac{E}{R} + A e^{-R/L t}$$

$$\theta = \tan^{-1} \left(\frac{\omega L}{R} \right) = \tan^{-1} \left(\frac{2\pi \cdot 50 \times 0.5}{5} \right) = 88.176^\circ$$

$$= 1.538$$

For $\omega t = \alpha$, $i = 0$ (initial condition)

$$A_1 = \frac{E}{R} - \frac{\sqrt{2} V_s}{Z} \sin(\alpha - \theta) e^{R/L \alpha / \omega}$$

Case (i) $\alpha = 30^\circ$

$$A_1 = 11.9556$$

for case (ii), $\alpha = 80^\circ$, $A_1 = 10.75$

for case (i), $i = \frac{\sqrt{2} V_s}{Z} \sin(\omega t - \theta) - \frac{E}{R} + 11.955 e^{-R/Lt}$

put $\omega t = \pi + \pi/6 = 7\pi/6$, $i = +ve$, current continuous


$i = 2.39 (+ve)$.

for case (ii), $i = \frac{\sqrt{2} V_s}{Z} \sin(\omega t - \theta) - \frac{E}{R} + 10.75 e^{-R/Lt}$

for $\omega t = 260^\circ$, $i = -ve$.

So current discontinuous.

④

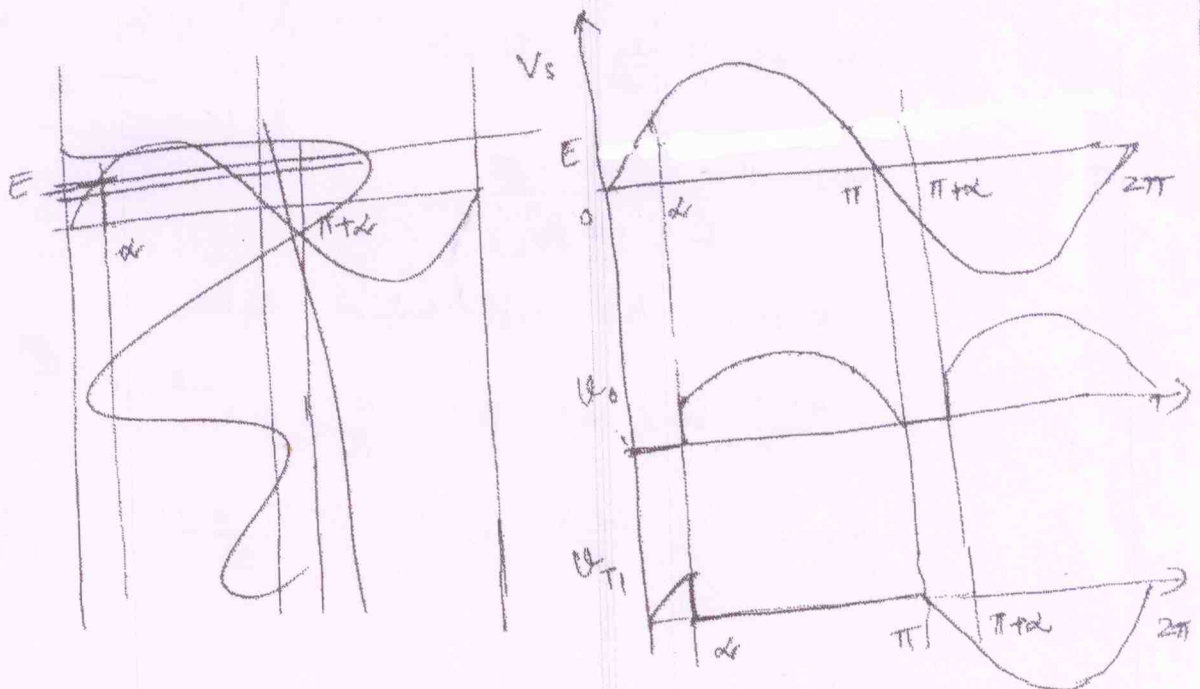

Conducting devices.

| $0 \text{ to } \alpha$ | $\alpha \text{ to } \pi$ | $\pi \text{ to } \pi + \alpha$ | $\pi + \alpha \text{ to } 2\pi$ |
|------------------------|--------------------------|--------------------------------|---------------------------------|
| D_1, D_2 | T_1, D_2 | D_1, D_2 | T_2, D_1 |

Q5.

$$I_{av} = \frac{1000}{100} = 10A$$

Average voltage drop across the inductor, L is zero.

$$\therefore \frac{2V_m}{\pi} \cos\alpha = 5 \times 10 + 100 = 150$$

$$\therefore \cos\alpha = \frac{150 \times \pi}{2 \times 240 \times \sqrt{2}} = 0.694$$

$$\therefore \alpha = 46.05^\circ$$