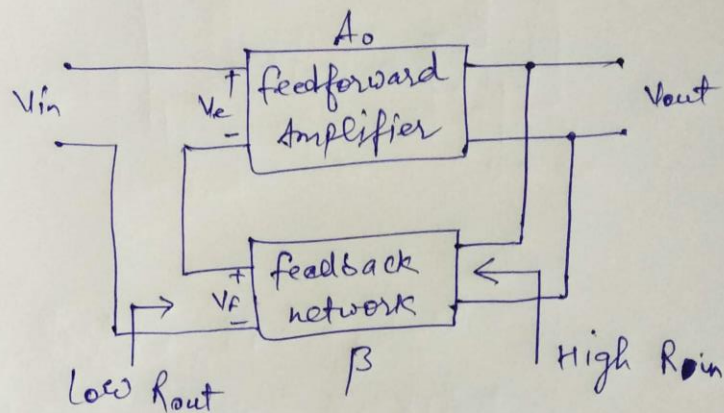


**EE 204-2018-2 Analog Circuits**  
**Homework #4 Solution**

**Question 1:**

Ques 1. [Chapter - 8  $\rightarrow$  Feedback, B. Razavi, Analog Circuits Book]  
Four types of feedback network  $\Rightarrow$

① Voltage-Voltage feedback  $\Rightarrow$



Here, feedback network is connected in parallel with the output and in series with the input port.

$$\therefore V_f = \beta V_{out}$$


$$V_e = V_{in} - V_f$$

$$\text{and } V_{out} = A_o (V_{in} - \beta V_{out})$$

Gain

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{A_o}{1 + \beta A_o}}$$

## Output Resistance

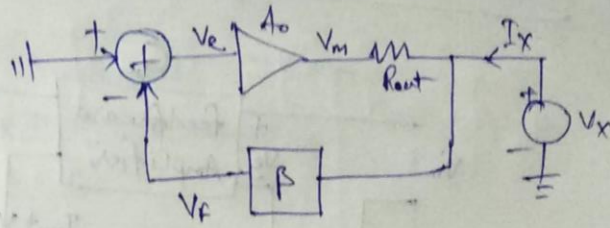

$R_{out}$  = output impedance of feedback amplifier.

$$V_f = \beta V_o$$

$$V_e = -\beta V_x$$

$$V_m = -\beta A_o V_x$$

Hence 
$$I_x = \frac{V_x - (-\beta A_o V_x)}{R_{out}}$$

$$\boxed{\frac{V_x}{I_x} = \frac{R_{out}}{1 + \beta A_o}}$$

## Input Resistance $\rightarrow$

$$V_e = I_x R_{in}$$

$$V_f = \beta A_o I_x R_{in}$$

we have


$$V_e = V_x - V_f$$

$$= V_x - \beta A_o I_x R_{in}$$

thus


$$I_x R_{in} = V_x - \beta A_o I_x R_{in}$$
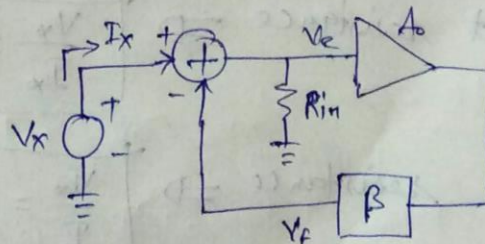
$$\boxed{\frac{V_x}{I_x} = R_{in}(1 + \beta A_o)}$$




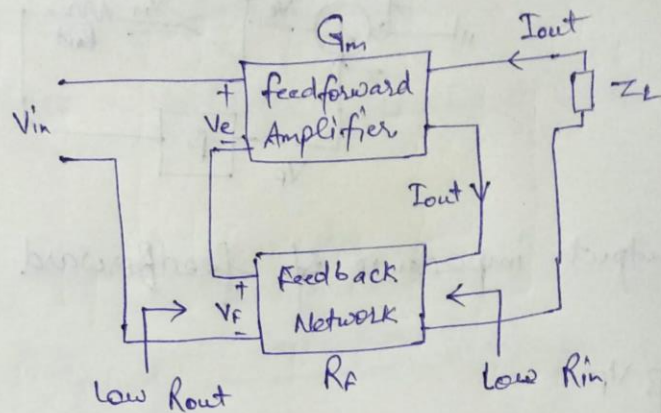
## ② Current-Voltage Feedback $\Rightarrow$



$$V_f = R_f I_{out}$$

$$V_e = V_{in} - R_f I_{out}$$

Hence

$$I_{out} = G_m (V_{in} - R_f I_{out})$$


$$\boxed{\frac{I_{out}}{V_{in}} = \frac{G_m}{1 + G_m R_f}}$$

Similarly as part ①,

output resistance  $\Rightarrow$   $\boxed{\frac{V_x}{I_x} = R_{out} (1 + G_m R_f)}$

Input resistance  $\Rightarrow$   $\boxed{\frac{V_x}{I_x} = R_{in} (1 + G_m R_f)}$
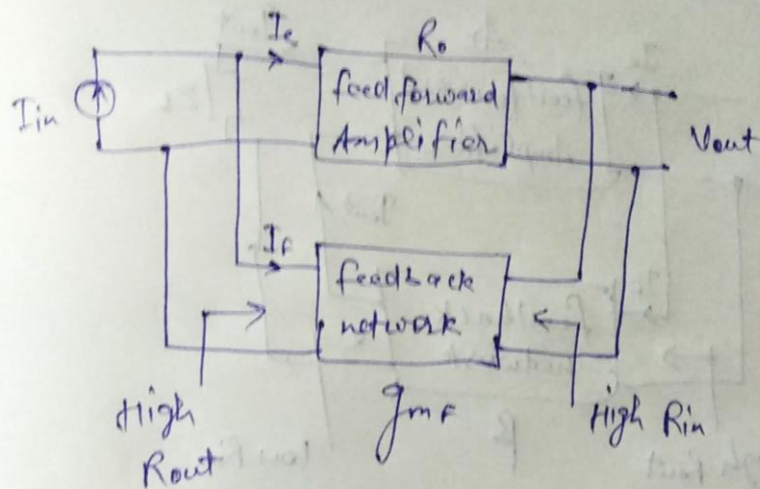
## ③ Voltage - Current feedback $\Rightarrow$



$$I_f = g_{mf} V_{out}$$

$$I_e = I_{in} - I_f$$

$$\Rightarrow V_{out} = R_o I_e = R_o (I_{in} - g_{mf} V_{out})$$


$$\boxed{\frac{V_{out}}{I_{in}} = \frac{R_o}{1 + g_{mf} R_o}}$$

Output ~~impedance~~ resistance  $\Rightarrow$   $\boxed{\frac{V_r}{I_r} = \frac{R_{out}}{1 + g_{mf} R_o}}$

Input resistance  $\Rightarrow$   $\boxed{\frac{V_r}{I_r} = \frac{R_{in}}{1 + g_{mf} R_o}}$


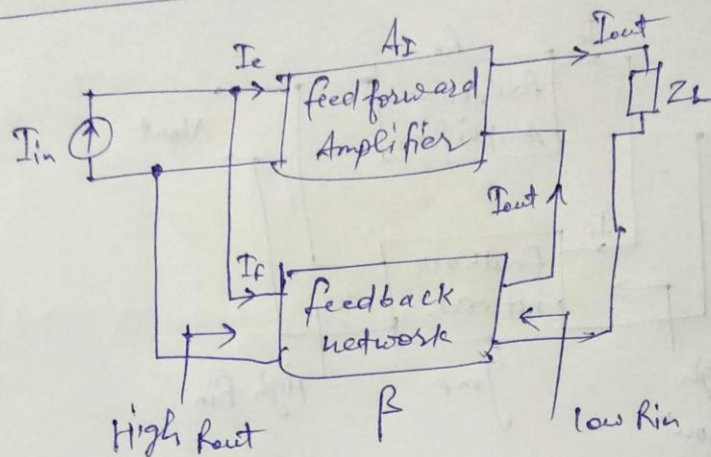
## ④ Current - Current feedback $\Rightarrow$



Gain  $\Rightarrow$  
$$\frac{I_{out}}{I_{in}} = \frac{A_I}{1 + \beta A_I}$$

Output resistance  $\Rightarrow$  
$$R_{out} (1 + \beta A_I)$$

Input resistance  $\Rightarrow$  
$$\frac{R_{in}}{1 + \beta A_I}$$


\* Note  $\Rightarrow$  You can refer "Design of Analog CMOS Integrated Circuits".

$\rightarrow$  Chapter - 8  $\Rightarrow$  feedback.

$\rightarrow$  B. Razavi

## Question 2:

Ques 2

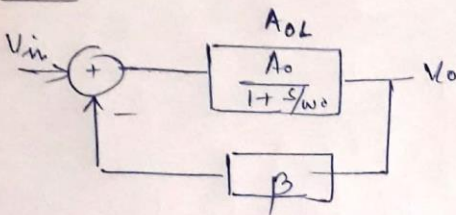

$$A_{OL} = \frac{A_0}{1 + \frac{s}{w_0}}$$

$$\frac{V_o}{V_{in}} = \frac{A}{1 + A\beta} = \frac{\frac{A_0}{1 + s/w_0}}{1 + \frac{\beta A_0}{1 + s/w_0}} = \frac{A_0}{1 + \frac{s}{w_0} + \beta A_0}$$

$$A_{CL} = \frac{\left[ \frac{A_0}{1 + A_0\beta} \right]}{\left[ 1 + \frac{s}{w_0(1 + A_0\beta)} \right]}$$

the cut-off freq has now become:  $w_0(1 + A_0\beta)$


⇒ Gain-Bandwidth product for open loop system at 3dB frequency.

$$\frac{A_0}{\sqrt{2}} \times w_0 = \frac{A_0 w_0}{\sqrt{2}}$$

Gain-Bandwidth product for closed loop system at 3dB frequency.

$$\frac{A_0}{(1 + A_0\beta)\sqrt{2}} \times w_0(1 + A_0\beta) = \frac{A_0 w_0}{\sqrt{2}}$$

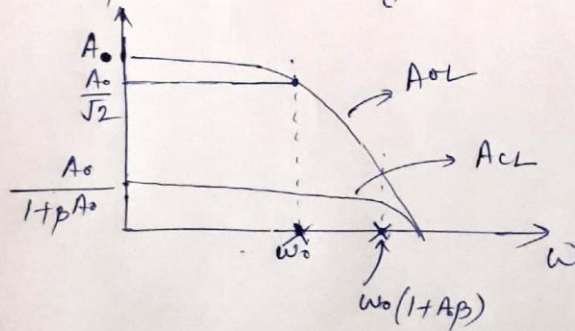Hence proved. that gain bandwidth product is constant.






#### Question 4:

##### Question 4


##### Part a)

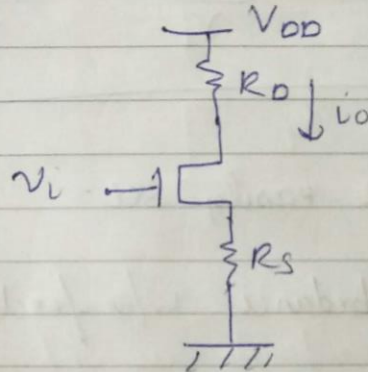

In the above circuit  $i_o$  creates a voltage difference across  $R_S$  which further changes  $v_{gs}$  across mosfet and acts as feedback.  $R_S$  is the feedback element.

The type is current - voltage feedback

For open-loop gain

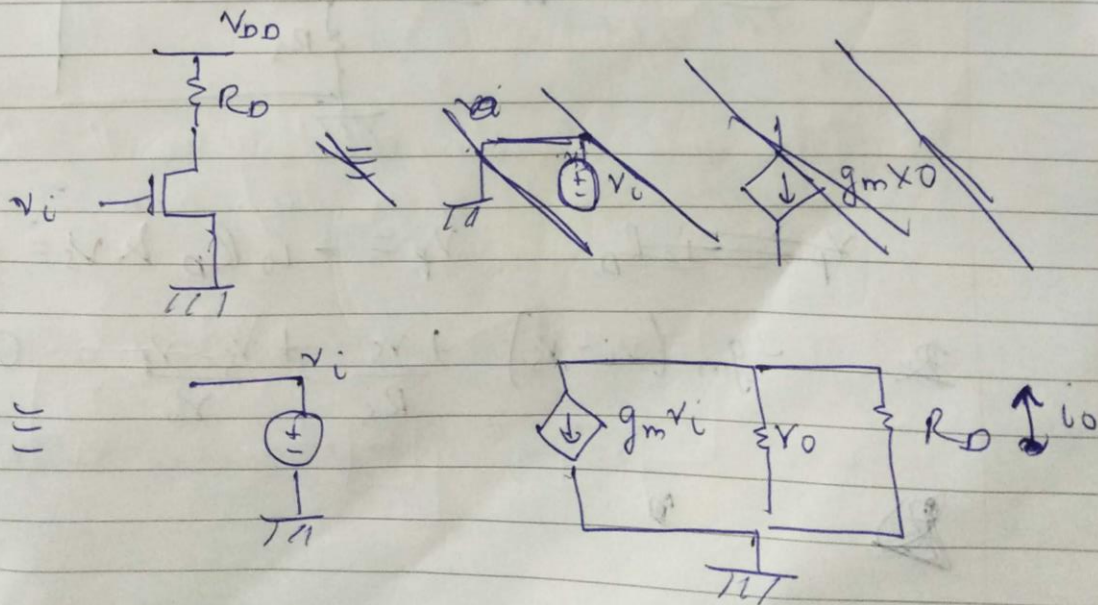

We get  $i_o = \pm g_m v_i \times \frac{r_o}{r_o + R_D}$


$$\Rightarrow A_v = \frac{i_o}{v_i} = \frac{+g_m r_o}{r_o + R_D}$$

From circuit we easily see -

Input impedance w/o feedback =  $\infty$

Output impedance w/o feedback =  $R_D \parallel r_o$

For closed loop gain we have

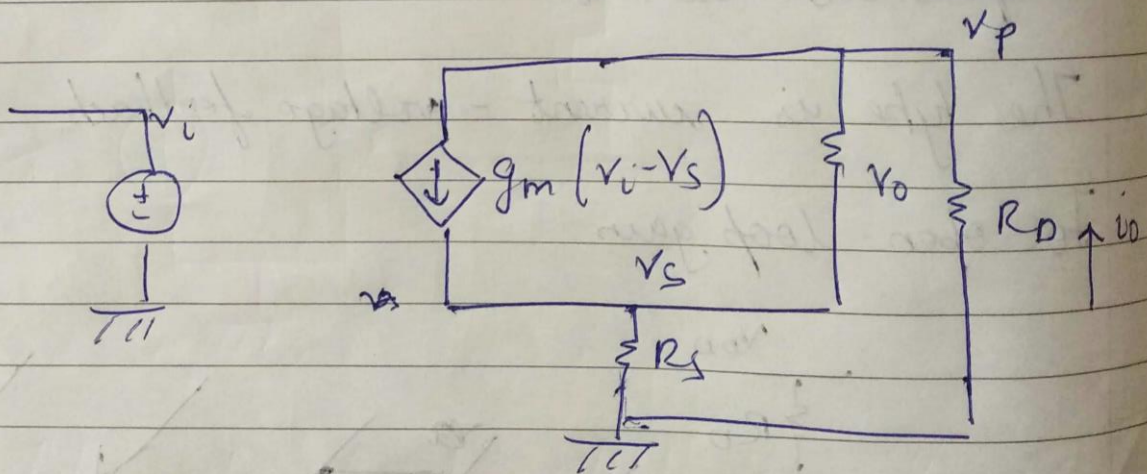

$$v_p = -i_o R_D$$

$$v_s = i_o R_S$$

$$-g_m (v_i - v_s) + \frac{v_s}{R_S} + \frac{v_s - v_p}{r_o} = 0$$



Date: youva

$$\Rightarrow -g_m (v_i - i_o R_s) + \frac{i_o R_s}{R_s} + \frac{i_o R_s + i_o R_D}{r_o} = 0$$

$$\Rightarrow g_m v_i = i_o \left( g_m R_s + 1 + \frac{R_s + R_D}{r_o} \right)$$


$$\Rightarrow \boxed{\frac{i_o}{v_i} = \frac{g_m r_o}{r_o + g_m R_s r_o + R_s + R_D}}$$

↓  
closed-loop gain

From the circuit we easily see

Input impedance with feedback =  $\infty$


For output impedance -

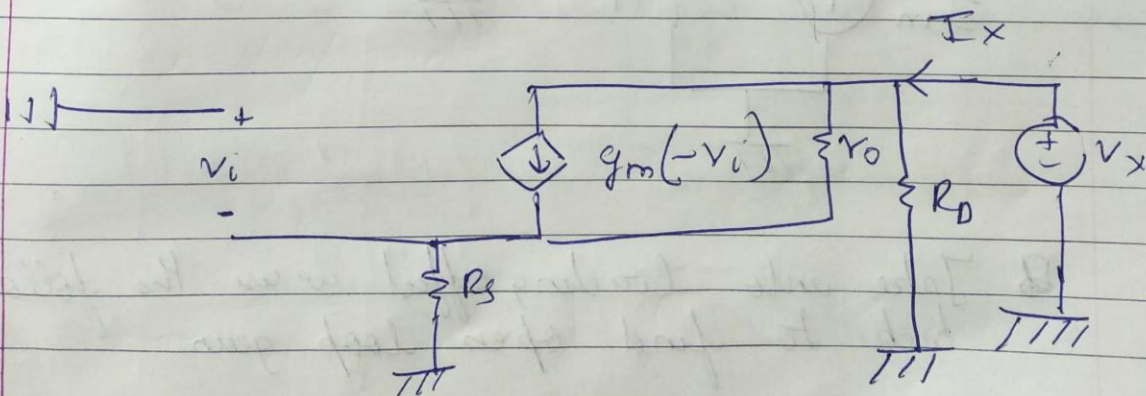

Solving above circuit we get


Output impedance with feedback =  $(r_o + g_m r_o R_s) \parallel R_D$

Part b)

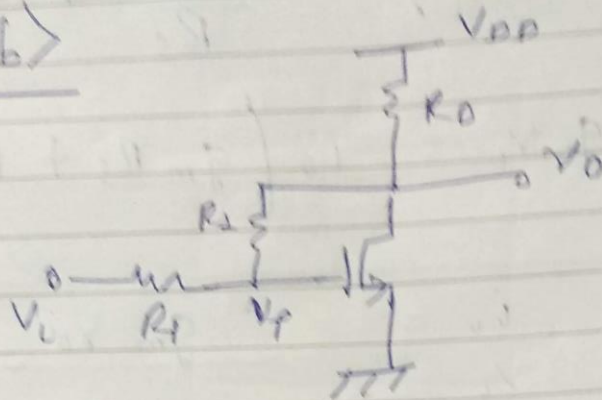


In the above case  $R_2$  senses output voltage & gives appropriate current at node P.

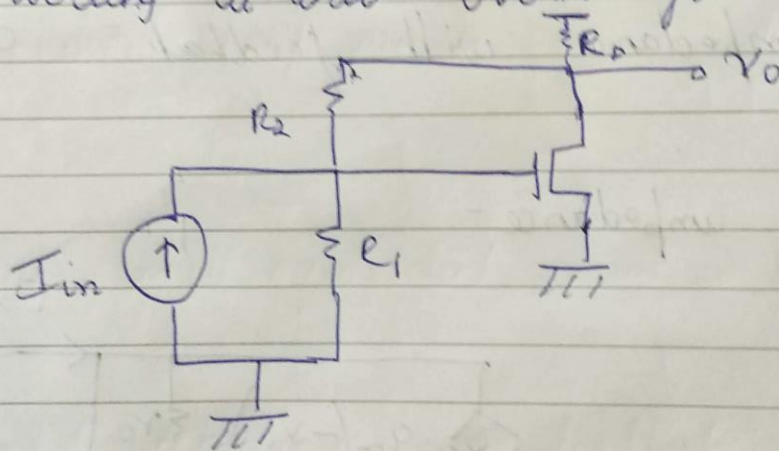The type is voltage-current feedback. Converting it into Norton form.





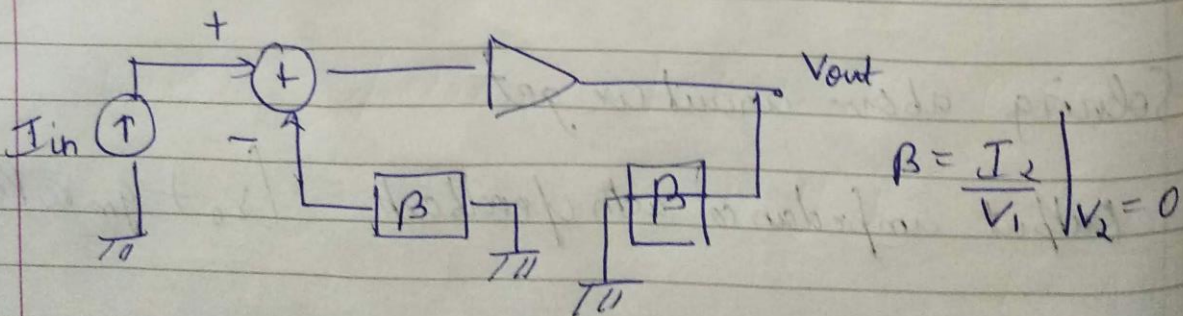Take into loading effect we use the following trick to find open loop gain





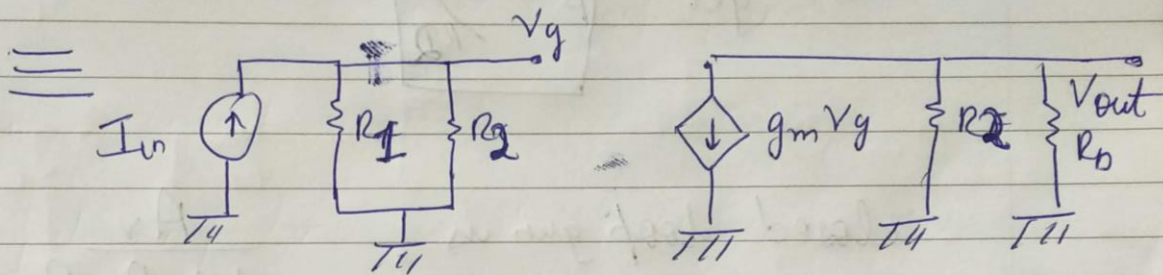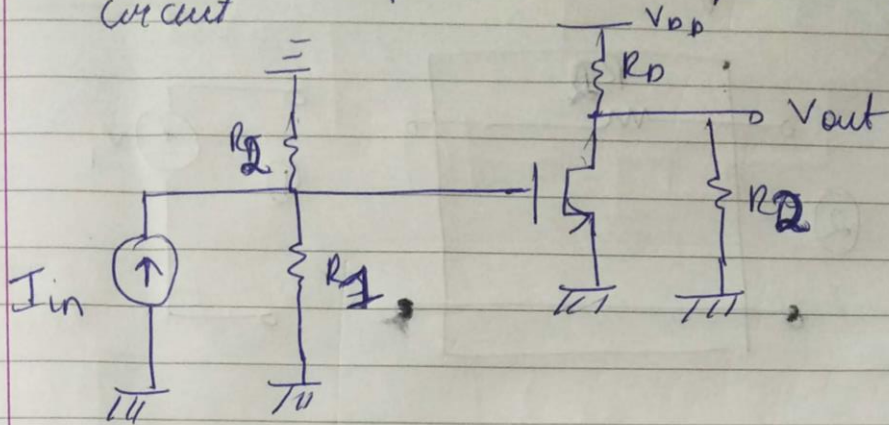We break the feedback loop and get the following circuit



$$V_{out} = -g_m V_g (R_2 \parallel R_D)$$

$$\& \quad V_g = I_{in} \times (R_1 \parallel R_2)$$


$$\therefore \quad \boxed{\frac{V_{out}}{I_{in}} = -g_m (R_1 \parallel R_2) (R_2 \parallel R_D)}$$

(A<sub>v</sub>)  $\downarrow$  ~~the~~ open loop gain

$$\& \quad \beta = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

where ① is looking into input of feedback and ② looking from output of feedback

We have the feedback circuit as

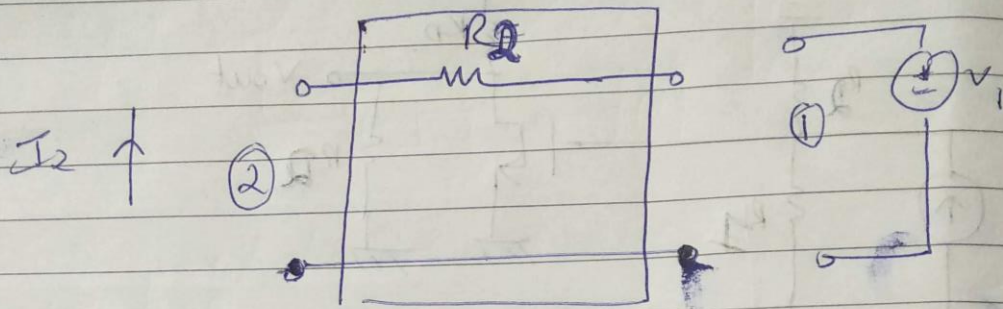

We get  $\beta = -\frac{1}{R_2}$

closed loop gain is  $\frac{A_v}{1 + A_v \beta}$

Now from small equivalent circuit we can easily see

Input impedance w/o feedback =  $R_1 \parallel R_2$


" " w feedback =  $\frac{R_1 \parallel R_2}{1 + A_v \beta}$

Output impedance w/o feedback =  $R_2 \parallel R_o$

" " w feedback =  $\frac{R_2 \parallel R_o}{1 + A_v \beta}$




Part c)

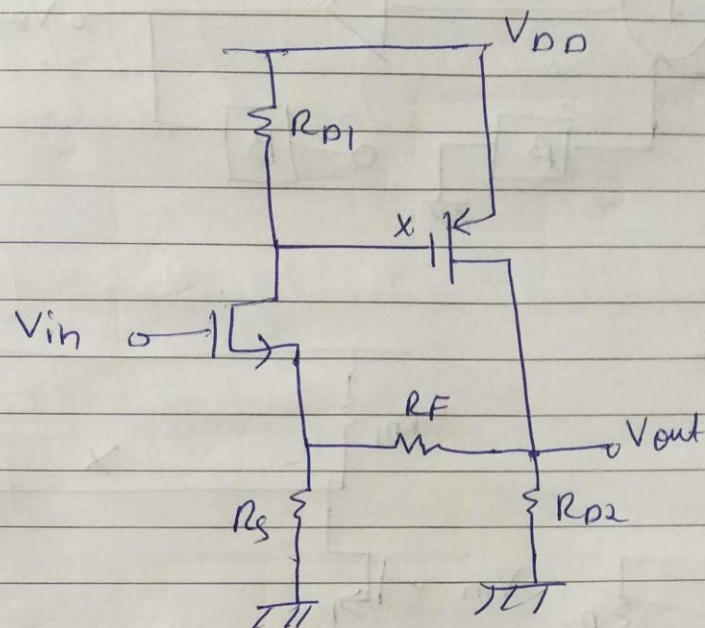


In the above circuit  $R_F$  and  $R_S$  senses output voltage and returns a fraction of it to the first MOSFET as  $V_{gs}$ .

The feedback circuit is


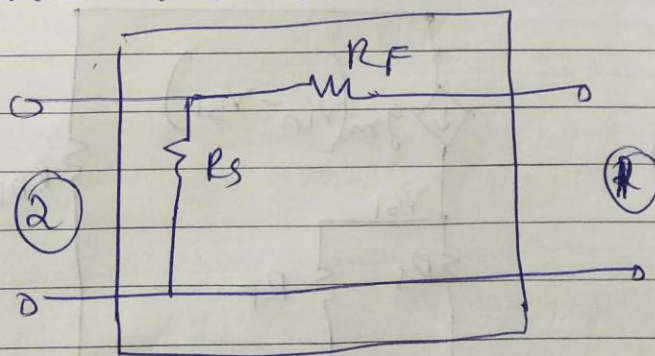


The type is voltage-voltage feedback

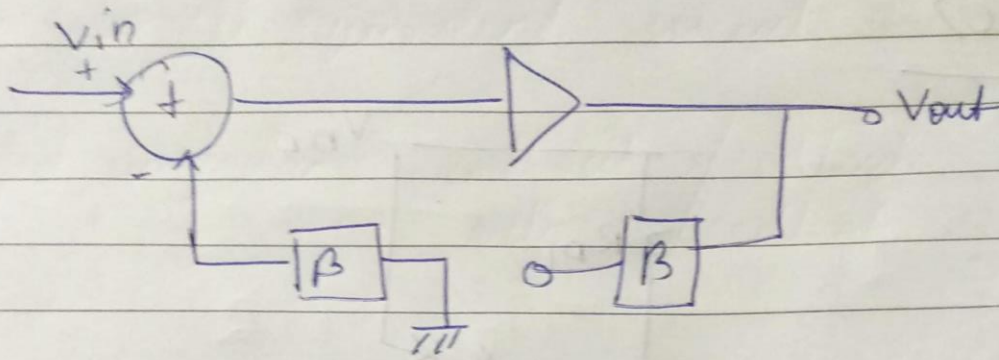We again use another trick for open-loop gain to take care of loading effect



we have

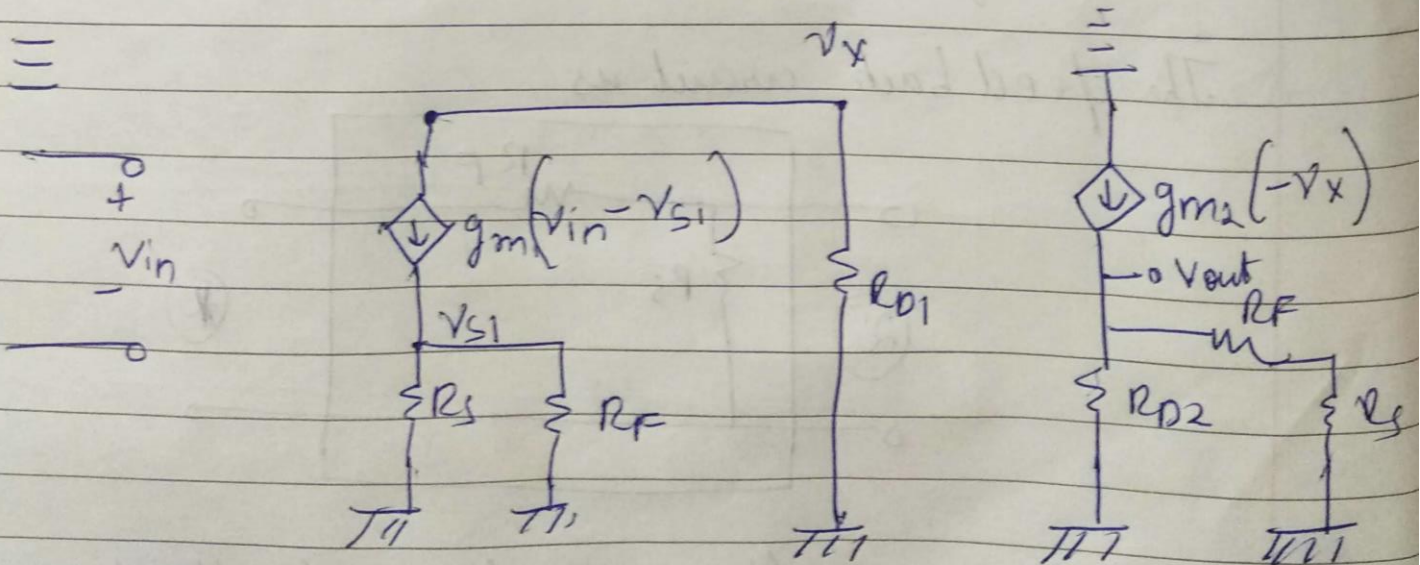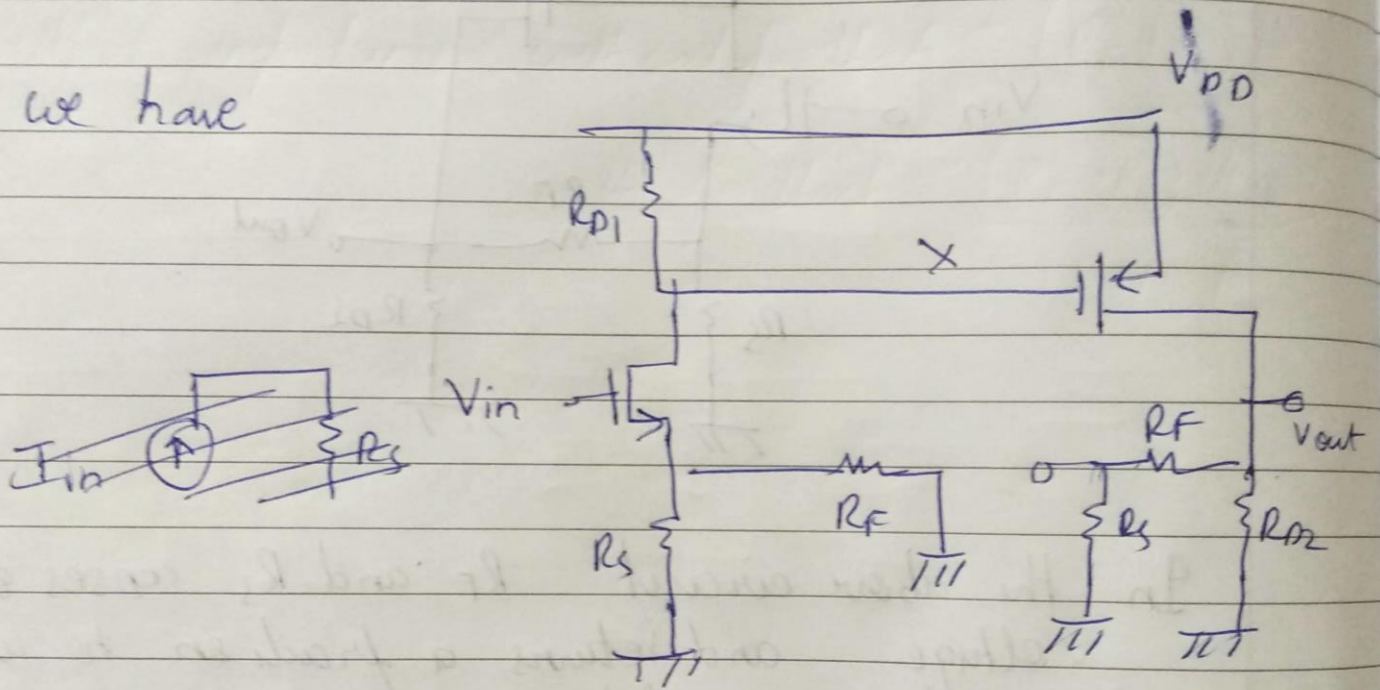



$$v_{s1} = g_{m1} (v_{in} - v_{s1}) (R_s \parallel R_F)$$

$$\Rightarrow v_{s1} (1 + g_{m1} (R_s \parallel R_F)) = g_{m1} v_{in} (R_s \parallel R_F)$$

$$\Rightarrow v_{s1} = \frac{g_{m1} v_{in} (R_s \parallel R_F)}{1 + g_{m1} (R_s \parallel R_F)}$$

And.

$$v_x = -g_{m1} (v_{in} - v_{s1}) R_{D1}$$

$$= - \frac{g_{m1} v_{in} R_{D1}}{1 + g_{m1} (R_s \parallel R_F)}$$

And.

$$v_{out} = g_{m2} (-v_x) (R_{D2} \parallel (R_s + R_F))$$

$$\boxed{\frac{v_{out}}{v_{in}} = - \frac{g_{m2} g_{m1} R_{D1} (R_{D2} \parallel (R_s + R_F))}{1 + g_{m1} (R_s \parallel R_F)}}$$

↓ open loop gain ( $A_v$ )

Again using  $\beta = \frac{V_2}{V_1} \Big|_{I_2=0} \Rightarrow \beta = \frac{R_s}{R_F + R_s}$

$$\therefore \text{closed loop gain} = \frac{A_v}{1 + A_v \beta}$$

From small equivalent circuit

$$\begin{array}{lll} \text{Input impedance} & \text{without feedback} & = \infty \\ \text{"} & \text{with feedback} & = \infty \end{array}$$


$$\text{Output impedance without feedback} = (R_F + R_S) \parallel R_{O2} \parallel r_o$$

$$\text{"} \quad \text{"} \quad \text{with feedback} = \frac{(R_F + R_S) \parallel R_{O2} \parallel r_o}{1 + A_v \beta}$$



# Question 5:

Ques 5

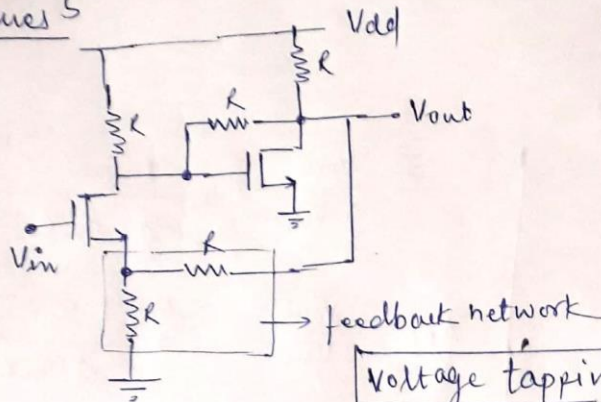

Given:  $\mu = \gamma = 0$

$$R = 2K\Omega$$

$$g_m = \frac{1}{200}$$

$$g_m R = 10$$


Voltage tapping & voltage mixing feedback


To solve for gain (closed loop), find out the open-loop gain first i.e.  $A_{OL}$  and then find out the  $\beta$  value.

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}, \quad \beta = \frac{R}{R+R} = \frac{1}{2} = 0.5$$

In order to find  $A_{OL}$ , we need to break the ckt in such a way so that there should be no loading effect and  $A_{OL}$  can be calculated easily.

[ kindly Refer to Razavi Book ]

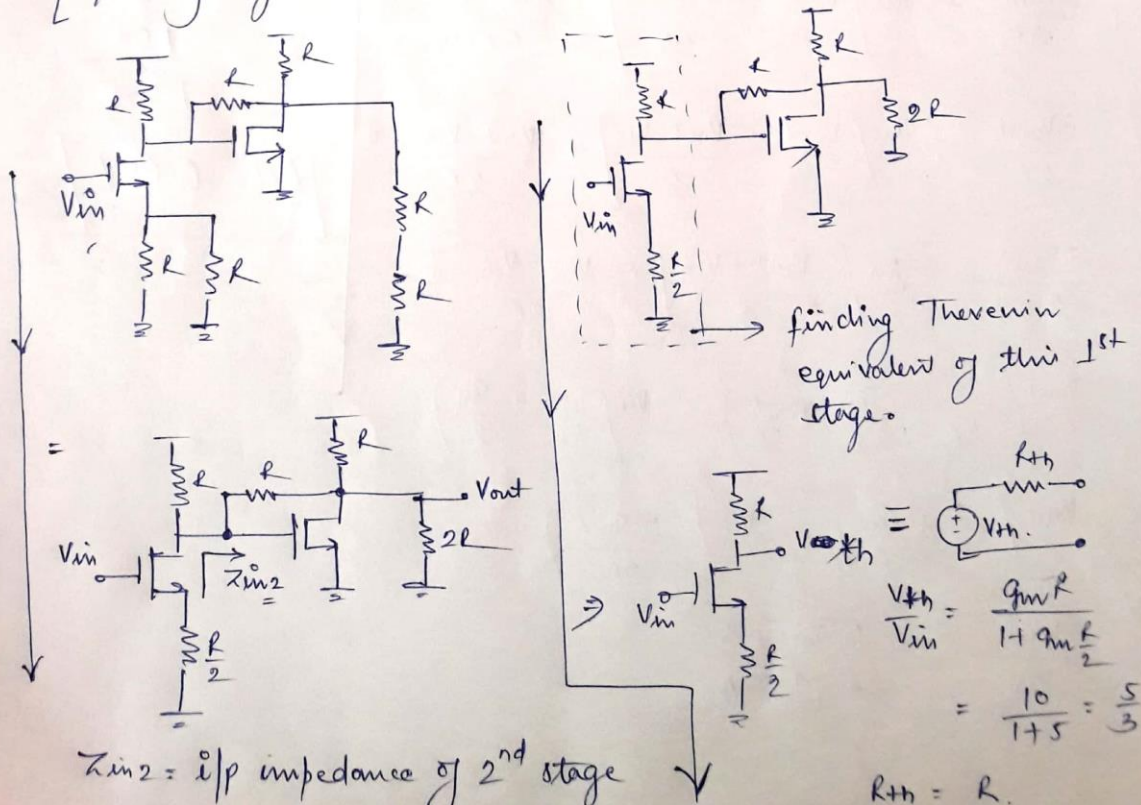


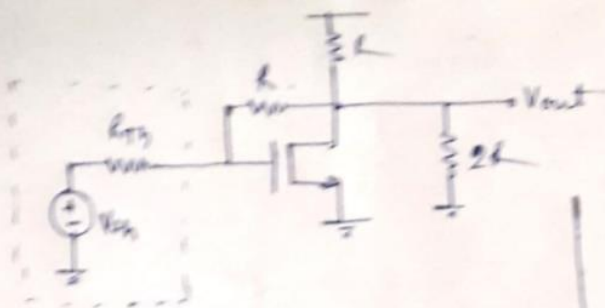

$$V_{TH} = \frac{5}{3} V_{in}$$

$$R_{TH} = R = 2k\Omega$$

applying small signal analysis.

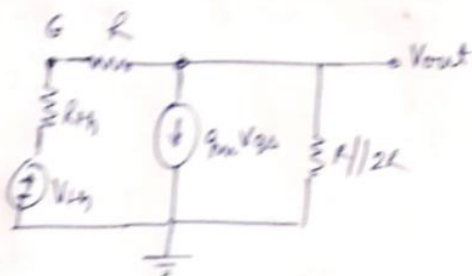

$$\frac{V_{out}}{2k} + g_m V_{be} + \frac{V_{out} - V_{TH}}{R + R_{TH}} = 0$$

$$\frac{3V_{out}}{2k} + g_m \left[ V_{out} - \frac{(V_{out} - V_{TH})R}{R + R_{TH}} \right] + \frac{V_{out} - V_{TH}}{R + R_{TH}} = 0$$

$$\frac{3V_{out}}{2k} + g_m \left[ V_{out} - \frac{V_{out} - V_{TH}}{2} \right] + \frac{V_{out} - V_{TH}}{2k} = 0$$

$$\frac{3V_{out}}{2k} + g_m \left[ \frac{V_{out} + V_{TH}}{2} \right] + \frac{V_{out} - V_{TH}}{2k} = 0$$

$$V_{out} \left[ \frac{3}{2k} + \frac{g_m}{2} + \frac{1}{2k} \right] = V_{TH} \left[ \frac{1}{2k} - \frac{g_m}{2} \right]$$

$$V_{out} \left[ \frac{2}{k} + \frac{g_m}{2} \right] = V_{TH} \left[ \frac{1 - g_m k}{2k} \right]$$

$$\frac{V_{out}}{V_{TH}} = \frac{(1 - g_m k) 2k}{2k (2 + g_m k)}$$

$$\Rightarrow \frac{V_{out}}{\frac{5}{3} V_{in}} = \frac{1 - g_m k}{4 + g_m k}$$

$$A_{OL} = \frac{V_{out}}{V_{in}} = \frac{5}{3} \frac{(1 - g_m k)}{4 + g_m k}$$

$$= \frac{5}{3} \times \frac{(1 - 10)}{4 + 10}$$

$$= \frac{5}{3} \times \frac{(-9)}{14} = -1.07$$

$$|A_{ocL}| = \frac{A_{ocL}}{1 + \beta A_{ocL}}$$

$$= \frac{1.07}{1 + 0.5(1.07)}$$


$$= \frac{1.07}{1.535}$$

$$A_{ocL} = 0.697$$



## Question 6:

Ques 6

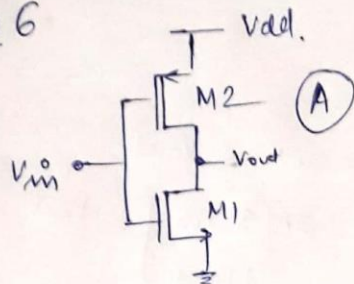

Q


$V_{gs}$  is same for both the transistor M1 & M2. ( $V_{gs} = V_{in}$ )

$$V_{out} = - (g_{m1} + g_{m2}) V_{gs} (r_{o1} || r_{o2})$$

$$= - (g_{m1} + g_{m2}) V_{in} (r_{o1} || r_{o2})$$

$$A_v = \frac{V_{out}}{V_{in}} = - (g_{m1} + g_{m2}) (r_{o1} || r_{o2})$$

output impedance.

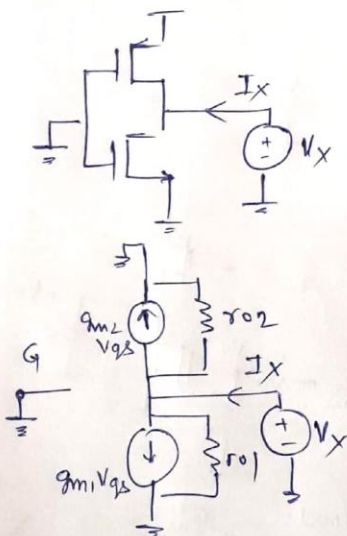


$$g_{m1} V_{gs} = g_{m2} V_{gs} = 0$$

$$\text{as } V_{gs} = 0$$

$$\frac{V_x}{I_x} = r_{o2} || r_{o1}$$

b sensitivity

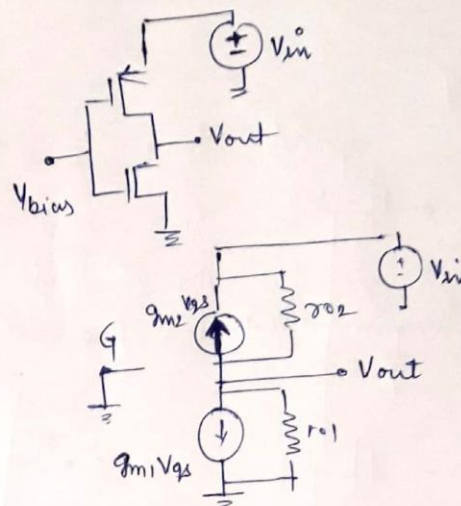

$$g_{m1} V_{gs} = 0 \quad \text{as } V_{gs} = 0$$

$$g_{m2} V_{gs} = g_{m2} [0 - V_{in}]$$

$$= - g_{m2} V_{in}$$


Applying KCL @ node Vout

$$\frac{V_{out}}{r_{o1}} + g_{m2} V_{gs} + \frac{V_{out} - V_{in}}{r_{o2}} = 0$$


$$\Rightarrow V_{out} \left( \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) = \frac{V_{in}}{r_{o2}} + g_{m2} V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{(1 + g_{m2} r_{o2})}{r_{o2}} (r_{o2} || r_{o1})$$


$$\text{sensitivity} \approx g_{m2} (r_{o2} || r_{o1})$$

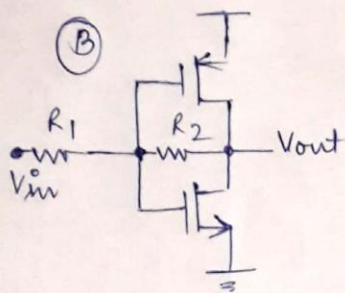

(a) Gain

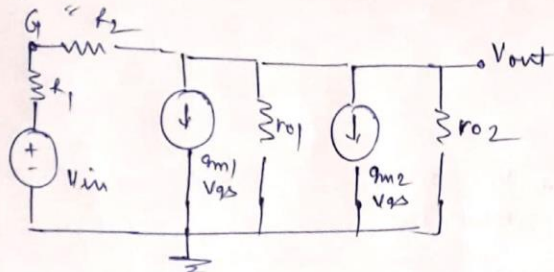

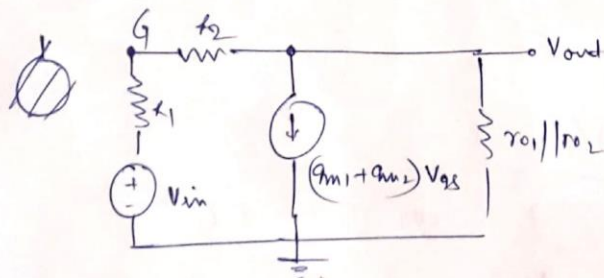Since  $v_{gs}$  is same for both NMOS & PMOS.



$$\frac{V_{out}}{r_{o1} || r_{o2}} + (g_{m1} + g_{m2})V_{gs} + \frac{V_{out} - V_{in}}{R_1 + R_2} = 0 \quad (1)$$

$$V_g = V_{out} - \frac{(V_{out} - V_{in})R_2}{R_1 + R_2}$$


$$V_g = \frac{V_{out}R_1 + V_{in}R_2}{R_1 + R_2} \quad (2)$$

solving (1) & (2)

$$\frac{V_{out}}{V_{in}} = \frac{1 - (g_{m1} + g_{m2})R_2}{(R_1 + R_2) \left[ \frac{1}{r_{o1} || r_{o2}} + \frac{(g_{m1} + g_{m2})R_1}{R_1 + R_2} + \frac{1}{R_1 + R_2} \right]}$$



Output impedance.

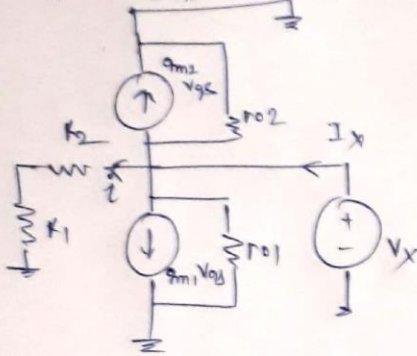

$$I_x = I + g_{m1}V_{gs1} + g_{m2}V_{gs2} + \frac{V_x}{r_{o1}} + \frac{V_x}{r_{o2}}$$

$$= \frac{V_x}{R_1 + R_2} + g_{m1} \left[ \frac{V_x R_1}{R_1 + R_2} \right] + g_{m2} \left( \frac{V_x R_1}{R_1 + R_2} \right) + \frac{V_x}{r_{o1}} + \frac{V_x}{r_{o2}}$$


$$\frac{I_x}{V_x} = \frac{1 + (g_{m1} + g_{m2})R_1}{R_1 + R_2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}$$

$$\frac{V_x}{I_x} = r_{o1} \parallel r_{o2} \parallel \frac{(R_1 + R_2)}{[1 + (g_{m1} + g_{m2})R_1]}$$

from eq 1 ① ② & ③

$$\frac{V_{out}}{V_{in}} = \frac{(g_{m2}r_{o2} + 1)(r_{o1} \parallel r_{o2}) \parallel \frac{R_2 + R_1}{1 + (g_{m1} + g_{m2})R_1}}{r_{o2}}$$

⑥ Sensitivity

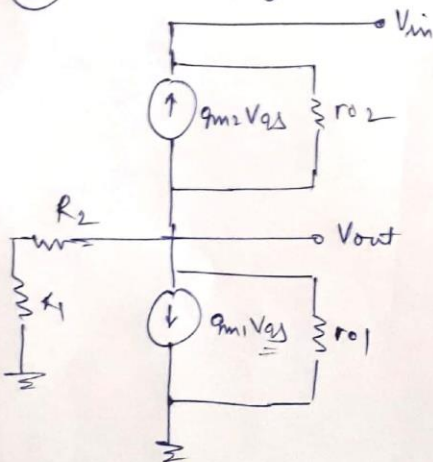

\* Ckt 2 is less sensitive


$$\frac{V_{out} - V_{in}}{r_{o2}} + \frac{V_{out}}{r_{o1}} + g_{m1}V_{gs1} + g_{m2}V_{gs2} + \frac{V_{out}}{R_1 + R_2} = 0 \quad \text{--- ①}$$

$$V_{gs1} = \frac{V_{out} R_1}{R_1 + R_2} \quad \text{--- ②}$$

$$V_{gs2} = \frac{V_{out} R_1}{R_1 + R_2} - V_{in} \quad \text{--- ③}$$

# Question 7:

Ques 7

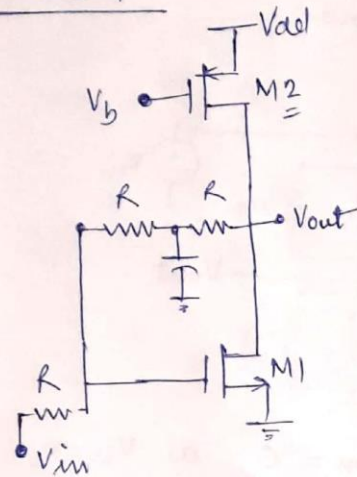


$$g_{m1,2} = \frac{1}{200} = g_m$$


$$R_{1,2} = 2k\Omega = R$$

ACL @ high & low frequencies.

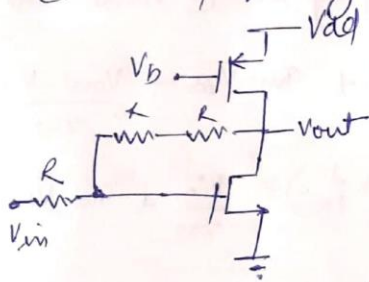- ① Gain @ very low frequency.  
The Capacitor will become open @ low frequency.



⇒ Small signal ckt

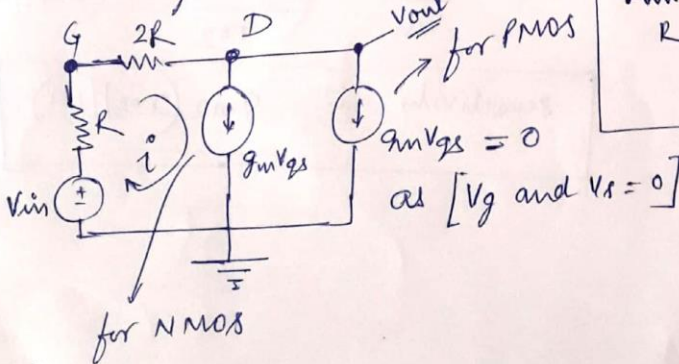

$$i = g_m v_{gs}$$

$$i = g_m [v_{in} - iR]$$

$$i = \frac{g_m v_{in}}{1 + g_m R}$$

$$v_{in} - 3iR = v_{out}$$



$$v_{in} - 3R \left[ \frac{g_m v_{in}}{1 + g_m R} \right] = v_{out}$$

$$v_{in} \left[ 1 - \frac{3R g_m}{1 + g_m R} \right] = v_{out}$$

$$\frac{v_{out}}{v_{in}} = \frac{1 - 2g_m R}{1 + g_m R}$$

$$= \frac{1 - 2 \times \frac{1}{200} \times 2000}{1 + \frac{1}{200} \times 2000} = \frac{-19}{11}$$

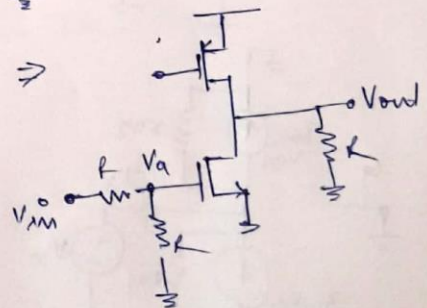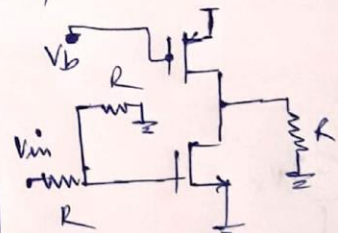- ② Gain @ very high frequency  
Capacitor will become short ckt



$$\frac{v_{out}}{v_a} = -g_m R$$

$$\frac{v_{out}}{\frac{v_{in}}{2}} = -g_m R$$

$$\frac{v_{out}}{v_{in}} = -\frac{g_m R}{2} = -5$$