

# EE214: Implementation to Finite State Machines

Madhav Desai

March 15, 2019

# A sequential system

- ▶ Sequences:  $\{x(k)\}, \{y(k)\}$  for  $k = 0, 1, 2, \dots$
- ▶ Sequential system: a map from sequences to sequences.

$$y(k+1) = y(k) \oplus x(k), \quad k \geq 0, \quad y(0) = y_0.$$

- ▶ Causal sequential system: a map  $F : X \rightarrow Y$  such that is  $\mathbf{x} = \{x(k)\} \in X$ , and  $\{y(k)\} = F(\mathbf{x})$ , then  $y(k)$  is determined only by  $x(0), x(1), \dots, x(k)$ .
- ▶ Finite memory sequential system.

# A Mealy machine

$$M = (\Sigma, \Lambda, Q, \delta, \lambda)$$

where

- ▶  $\Sigma$  is a finite set of input symbols.
- ▶  $\Lambda$  is a finite set of output symbols.
- ▶  $Q$  is a finite set of states.
- ▶  $\delta : \Sigma \times Q \rightarrow Q$  is a next-state function.
- ▶  $\lambda : \Sigma \times Q \rightarrow \Lambda$  is the output function.

## A Mealy machine: relations

$$\begin{aligned}q(k+1) &= \delta(x(k), q(k)) \\ y(k) &= \lambda(x(k), q(k))\end{aligned}$$

## A Mealy machine: an example

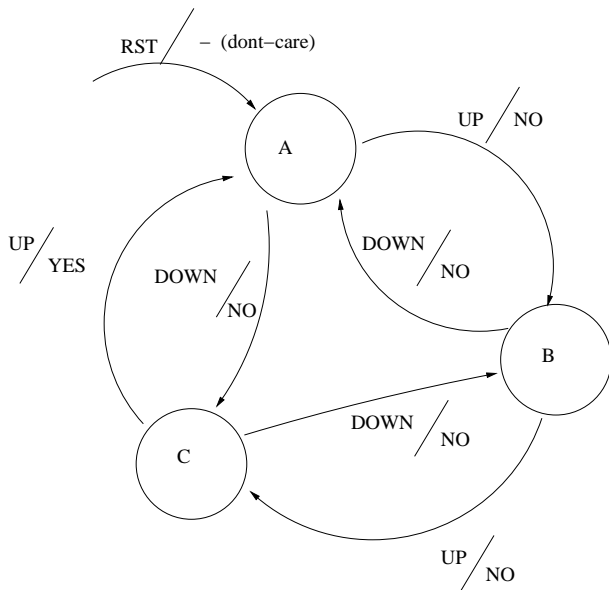


Figure: A simple FSM

# The Mealy machine: implementation

We need to define the instants  $k = 0, 1, 2, \dots$ . Use a periodic square wave.

 


Figure: Clock

# The Mealy machine: implementation

Symbols mapped to Boolean variables (encoding).

Input variables  $r$   $u$

Input coding  $RST \rightarrow 1_$ ,  $Up \rightarrow 01$ ,  $Down \rightarrow 00$

State variables  $q1$   $q0$

State coding  $A \rightarrow 00$ ,  $B \rightarrow 01$ ,  $C \rightarrow 10$

Output variables  $y$

Output coding  $YES \rightarrow 1$ ,  $NO \rightarrow 0$

# The Mealy machine: implementation

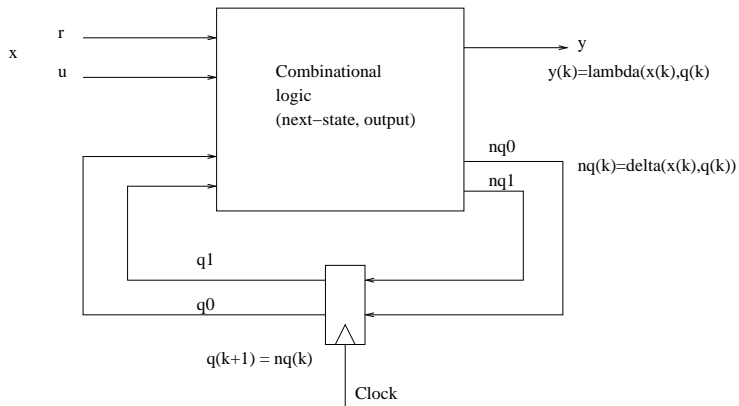



Figure: FSM Implementation



# Vhdl Description of the FSM

- ▶ Minimize the next state and output functions and implement using logic gates. Connect up everything (using flip-flops).
- ▶ Implement using variables (`FsmWithVars.vhdl`).
- ▶ Implement using symbols (`FsmWithSymbols.vhdl`).

# Timing Diagram

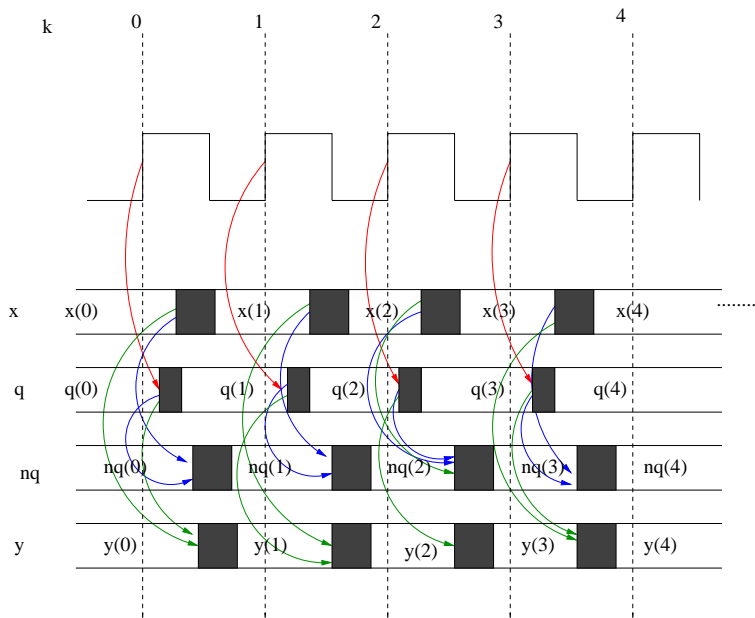

# Trace file construction

inputs

clock=0 x(0)

clock=1 x(0)

clock=0 x(1)

clock=1 x(1)

clock=0 x(2)

clock=1 x(2)

etc...

outputs

y(0)

ignore

y(1)

ignore

y(2)

ignore

# From specification to implementation

- ▶ Input-symbols are  $(RST, a, b)$ .
- ▶ Output-symbols are  $(match, nomatch)$ .
- ▶ The output sequence  $y(k) = match$  if and only if the sequence  $x(k-3)x(k-2)x(k-1)x(k)$  is either *abab* or *baba*.

# How to go about it?

- ▶ Identify the set of states.
- ▶ Build the state transition graph of the FSM.
- ▶ Implement the FSM using VHDL.
- ▶ Write a test trace file which ensures that every arc in the state transition graph is taken.