

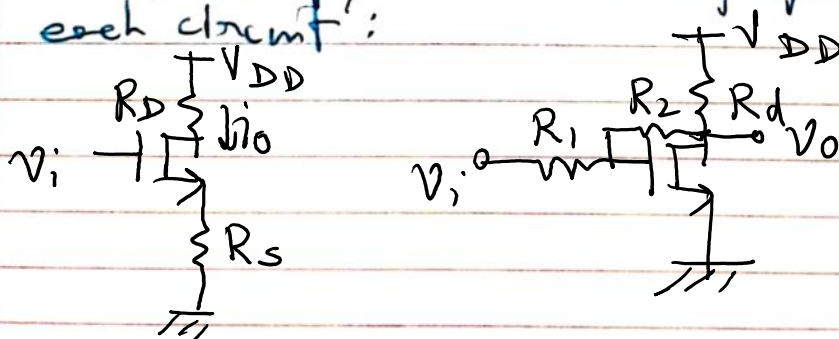


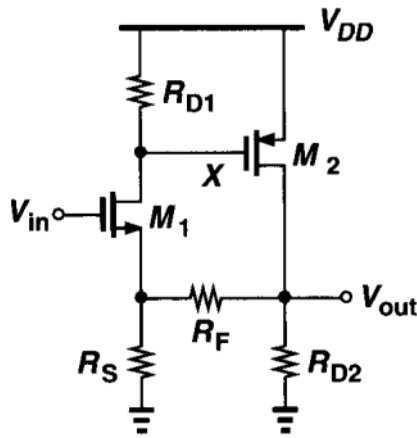1. Consider four types feedback networks ~~is~~ and find out the change in input resistance, output resistance and gain each case.
2. Show that negative feedback can increase the cut-off frequency of a low pass filter keeping the gain-bandwidth product constant.
3. Consider the gain block as a two port network... Similarly consider the feedback network as a two port network. Find out gain with feedback for all ^{four} types of feedback networks.
4. Find out the ~~gain~~ open loop gain, input and output impedances w/ and w/o feedback for the following circuits. Also, identify the nature of feedback in each circuit:





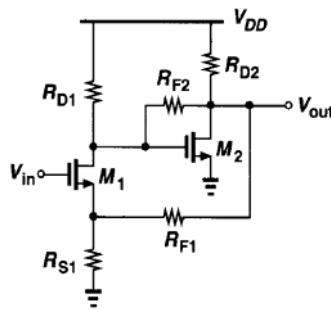

5. In the circuit of Fig. 8.63, suppose all resistors are equal to $2\text{ k}\Omega$ and $g_{m1} = g_{m2} = 1/(200\text{ }\Omega)$. Assuming $\lambda = \gamma = 0$, calculate the closed-loop gain and output impedance.



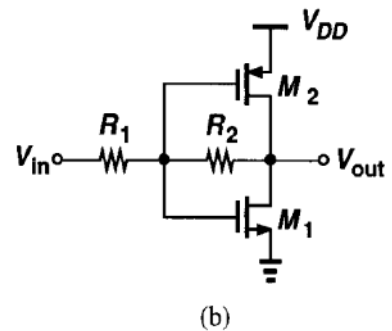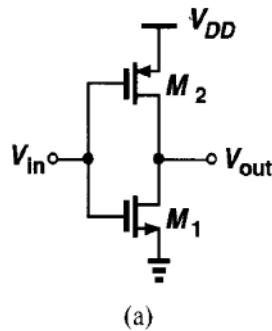6. 8.20. A CMOS inverter can be used as an amplifier with or without feedback (Fig. 8.64). Assume $(W/L)_{1,2} = 50/0.5$, $R_1 = 1\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, and the dc levels of V_{in} and V_{out} are equal.
- Calculate the voltage gain and the output impedance of each circuit.
 - Calculate the sensitivity of each circuit's output with respect to the supply voltage. That is, calculate the small-signal "gain" from V_{DD} to V_{out} . Which circuit exhibits less sensitivity?



7.

In the circuit of Fig. 8.66, assume $\lambda = 0$, $g_{m1,2} = 1/(200\ \Omega)$, $R_{1-3} = 2\ \text{k}\Omega$, and $C_1 = 100\ \text{pF}$. Neglecting other capacitances, estimate the closed-loop voltage gain at very low and very high frequencies. (5+5)

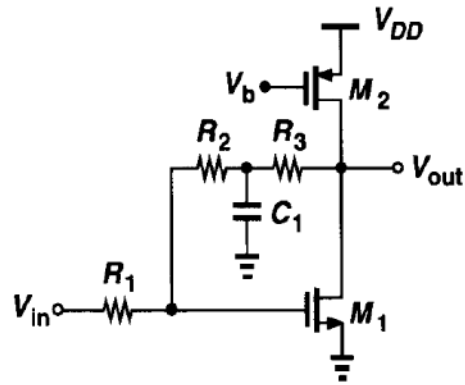


Figure 8.66