EE224 Handout Construction of a D Flip-flop

Madhav P. Desai

April 3, 2018

In this write-up we summarize the construction of an edge triggered D flip-flop, starting from logic gates, moving on to level triggered latches and ending with an edge triggered flip-flop. We will also quantify the setup time, hold time and delays of these circuits.

1 A memory element

To build a memory element, we must have a combinational loop in a logic circuit (why?). The simplest such circuit is the one shown in Figure 1. This circuit has two stable states: $Q=1, \overline{Q}=0$ and $Q=0, \overline{Q}=1$. To make the memory element usable, we need a mechanism to force values into the memory element. This can be done by using the SR-bistable circuit shown in Figure 2, in which Q and \overline{Q} can be controlled using the inputs $\overline{S}, \overline{R}$.

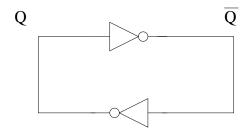


Figure 1: Back-to-back inverter loop

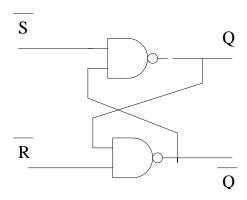


Figure 2: SR Bi-stable

In the SR-bistable, we observe the following excitation table:

\overline{S}	\overline{R}	Q	\overline{Q}
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q_{last}	\overline{Q}_{last}

To force the state $Q=0, \overline{Q}=1$, we make $\overline{S}=1, \overline{R}=0$ and to force the state $Q=1, \overline{Q}=0$, we make $\overline{S}=0, \overline{R}=1$. To hold the current state, we make $\overline{S}=\overline{R}=1$. The input combination $\overline{S}=\overline{R}=0$ is not used because if we go from this input combination to the hold input combination $\overline{S}=\overline{R}=1$, the values at Q, \overline{Q} are unpredictable (they depend on the relative delays of the two NAND gates).

To summarize, the SR-bistable allows us to store a bit of information using a pair of controlling signals \overline{S} and \overline{R} .

How about the timing of the latch? To force Q = 1, we must make $\overline{S} = 0$ and $\overline{R} = 1$. For how long must we hold the forcing input $\overline{S} = 1$? We must hold it low until \overline{Q} becomes 0, because after this happens, the output of the upper NAND gate remains 1 even if we make $\overline{S} = \overline{R} = 1$. Thus, the minimum duration for which \overline{S} must be held low in order to force Q = 1 is $(d_1 + d_2)$.

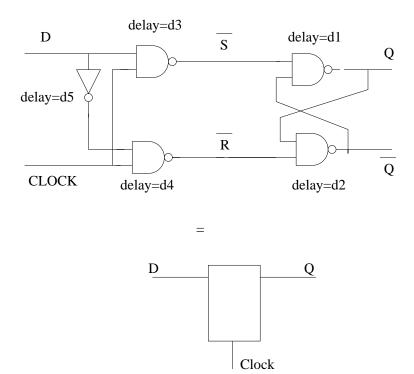


Figure 3: Positive level triggered latch

2 Level triggered latches

From the SR-bistable, we can construct a simple clocked memory circuit known as the positive level triggered D latch (see Figure 3). In this latch it is easy to see that if Clock = 1, then Q = D, and if Clock = 0, then $Q = Q_{last}$.

How do we characterize the timing of this latch? First of all we observe that the sampling edge is the falling edge of clock. Thus, we will calculate setup and hold times relative to the falling edge of the clock.

• If we wish to force Q=1, D must be held 1 long enough while clock is 1. When D=Clock=1, we will have $\overline{S}=0$ which will make Q=1. Note that if Clock goes from 1 to 0 at t_0 , then \overline{S} will stay at 0 until t_0+d_3 . To ensure that Q stays 1 after Clock goes to 0, we must ensure that \overline{S} remains 0 until \overline{Q} has changed to 1 so that the feedback loop has completely evaluated. Note that \overline{Q} depends on Q as well as on \overline{R} . Now if $D \uparrow$ at t=0, then $Q \uparrow$ at t=0 and t=0 and t=0. Thus, the

latest that $\overline{Q} \downarrow$ is at $t_1 = \max(d_3 + d_1 + d_2, d_5 + d_4 + d_2)$ (because \overline{Q} depends on Q with a delay of d_2 , and on \overline{R} with a delay of d_2). Thus we must ensure that $\overline{S} = 0$ until $t = t_1$. Since $\overline{S} \uparrow$ at $t_0 + d_3$, it follows that the setup time is at least $t_1 - d_3$, that is:

$$S_1 = \max(d_1 + d_2 + d_3, d_2 + d_4 + d_5) - d_3$$

See Figure 4 for a visualization.

• If we wish to force Q=0, \overline{D} must be held 1 long enough while clock is 1 so that the feedback loop is complete (that is, until Q becomes 1). Using the same argument as above, we observe that Q depends on \overline{S} as well as \overline{Q} . The latest that $Q \downarrow$ is at $t_2 = \max(d_1 + d_3, d_1 + d_2 + d_4 + d_5)$. We need to ensure that \overline{R} is held low until $t = t_2$. Observe that $\overline{R} \uparrow$ at $t = t_0 + d_4$. Thus, the setup time in this case is at least

$$S_2 = \max(d_1 + d_3, d_1 + d_2 + d_4 + d_5) - d_4$$

See Figure 4 for a visualization.

From this discussion, we conclude that if we change D and if we wish that this change is to sampled correctly into the latch, then we must allow a setup time of $\max(S_1, S_2)$.

Note: If the delays of all gates are equal (say, 1 unit) then the setup time of this latch is 3 units. Further, if we assume (as is typical), that $d_3 = d_4$ and $d_5 < d_3, d_4, d_1, d_2$, then the setup time is $d_1 + d_2 + d_5$.

How about the hold time? We observe that as soon as Clock goes to 0, the wires and \overline{S} and \overline{R} are no longer influenced by D, and consequently, we can change D without affecting Q. That is, the hold time of this latch is 0.


The positive level triggered latch is also called an A-latch, its setup time is thus $S_A = (d_1 + d_2 + d_5)$, and its hold time is $H_A = 0$. The two paths from D to Q have delays $d_1 + d_3$ and $d_1 + d_2 + d_4 + d_5$ respectively. Thus,

$$d_{D\to Q,A} \in [min(d_1+d_3,d_1+d_2+d_4+d_5), max(d_1+d_3,d_1+d_2+d_4+d_5)]$$

Similarly

$$d_{Clock \to Q, A} \in [min(d_1 + d_3, d_1 + d_2 + d_4), max(d_1 + d_3, d_1 + d_2 + d_4)]$$

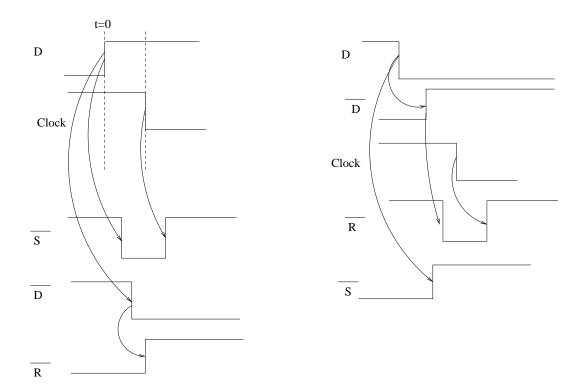By adding an inverter in the clock path, we obtain the negative level triggered latch shown in Figure 5. We see that Q follows D when Clock = 0



Timing Diagrams for Setup calculation

Figure 4: Timing diagram for setup calculation

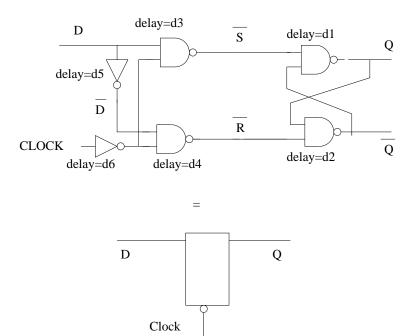


Figure 5: Negative level triggered latch

and when Clock = 1, Q remembers the last value it had at the point that Clock went from 0 to 1. The sampling edge for this is the positive edge of clock. So the B-latch can be analyzed exactly like the A-latch, but assuming that the sampling edge is delayed by an amount of d_6 . It is thus easy to see that the setup-time of the B-latch is $S_B = S_A - d_6$ and the hold-time of the B-latch is $H_B = d_6$.

For the B-latch, the two paths from D to Q have delays d_1+d_3 and $d_1+d_2+d_4+d_5$ respectively. Thus,

$$d_{D\to Q,B} \in [min(d_1+d_3,d_1+d_2+d_4+d_5), max(d_1+d_3,d_1+d_2+d_4+d_5)]$$

Similarly

$$d_{Clock \rightarrow Q, B} \in [min(d_1 + d_3 + d_6, d_1 + d_2 + d_4 + d_6), max(d_1 + d_3 + d_6, d_1 + d_2 + d_4 + d_6)]$$

3 Master-Slave D flip-flop

Using a cascade of a B-latch followed by an A-latch, one can construct a D-flipflop (see Figure 6). To see that this circuit functions as a D-flipflop,

observe that

- When Clock is 0, the net X follows D.
- At the instant that Clock switches from 0 to 1, X will contain the value of D, of course assuming that D is not changing at this instant (which it will not be, because D must satisfy the setup requirement).
- After *Clock* becomes 1, Q will follow X, which holds the value which D had at the rising edge of clock.
- Thus, Q will contain the value of D sampled by the rising edge of Clock.
- Notice that there is never a direct path from D to Q.

What about the timing of the master-slave D-flipflop? Look at the Figure in 7. One clock cycle of activity is shown. The following points are marked with dashed lines

- At t = 0, Clock falls from 1 to 0.
- The line at t_{HA} marks the boundary of the hold region for the A-latch.
- The line at t_D marks the time at which D changes.
- The line t_X marks the time at which X changes.
- The line at t_{SB} marks the boundary of the setup region for the B-latch.
- The line at t_{HB} marks the boundary of the hold region for the B-latch.
- The line at t_{SA} marks the boundary of the setup region for the A-latch.

For correct operation:

- We must have $t_D \leq t_{SB}$ for the change in D to be setup correctly to be captured by the B-latch.
- We must have $t_D \geq t_{HB}$ for the change in D to not be captured or influence the B-latch.

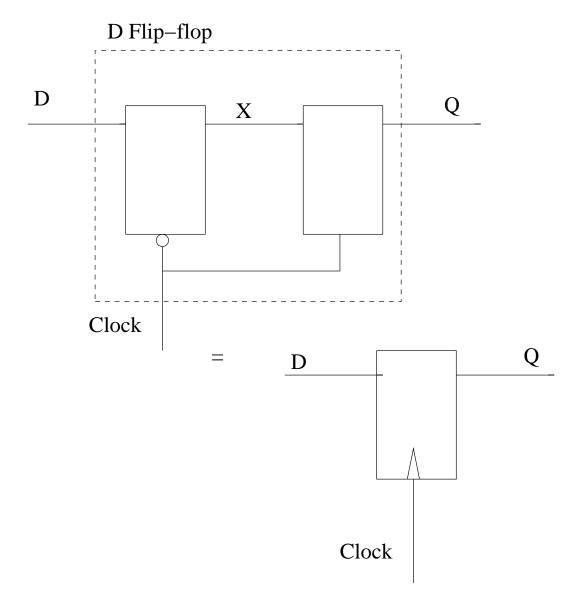


Figure 6: Master-Slave D flip-flop

• We must have $t_X \geq t_{HA}$ for the change in X to not influence the A-latch. The minimum possible value for t_X is $d_{Clock \to Q,B}$. Thus, we must have

$$d_{Clock \to Q,B} \ge H_A$$

for the flip-flop to work correctly.

• We must have $t_X \leq t_{SA}$ for the change in X to be correctly captured by the A-latch. The maximum possible value for t_X is $t_{SB} + d_{D \to Q,B}$. Thus, we must have

$$T/2 - S_B + d_{D \to Q,B} \le T - S_A$$

that is

$$d_{D\to Q,B} + (S_A - S_B) \le T/2$$

for the flip-flop to work correctly at clock period T.

The last two conditions are necessary for correct operation of the flip-flop. The first two conditions give us the setup and hold time of the flip-flop, which turn out to be S_B and H_B respectively.

How about the $Clock \to Q$ delay of the flip-flop? The earliest that Q can change will be $(T/2) + d_{Clock \to Q,A}$, because the A-latch opens at T/2. The latest time at which Q can change is determined by the latest time at which X can change. Note that X changes late if D changes as late. The latest that D can change is at t_{SB} , and consequently, the latest that X can change is $t_{SB} + d_{D \to Q,B}$. Thus, the latest that Q can change is

$$t_Q^{max} = t_{SB} + d_{D \to Q,A} + d_{D \to Q,B}$$

= $((T/2) - S_B) + d_{D \to Q,A} + d_{D \to Q,B}$
= $T/2 + (d_{D \to Q,A} + (d_{D \to Q,B} - S_B))$

Thus, we conclude that for the flip-flop

$$t_{Clock \to Q} \in [d_{Clock \to Q,A}, d_{Clock \to Q,A} + (d_{Clock \to Q,B} - S_B)]$$

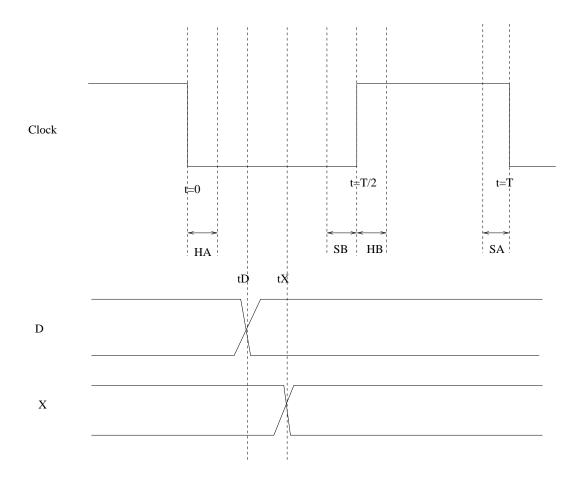


Figure 7: Timing analysis of the Master-Slave D flip-flop

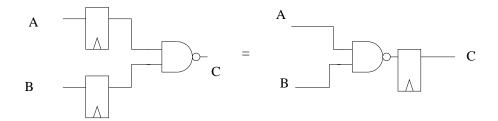


Figure 8: Retiming a circuit by moving D flip-flops

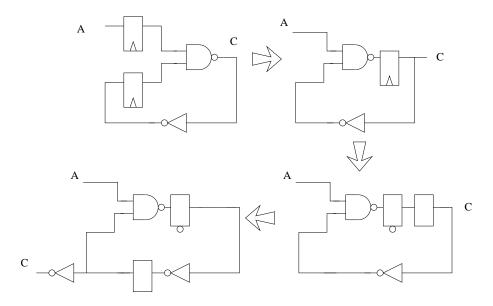


Figure 9: Retiming a circuit by moving latches

4 Retiming

It is possible to move flip-flops around in order to improve the circuit performance while preserving the functionality. For example, in Figure 8, the two circuits shown are identical functionally (in both cases, $C(k+1) = \overline{A(k).B(k)}$), but the timing of the two circuits different.

This concept can be taken further with latches as well. The circuit transformations shown in Figure 9 preserve circuit functionality but alter its timing.

Retiming of this kind is a powerful tool in the design of fast circuits. We will not study it further in this course, but its good to be aware of it.

5 Assignment

Consider the positive level triggered latch, negative level triggered latch, and the master-slave D flip-flop introduced earlier. Assume that the delay of each gate used in the positive level triggered latch is x units, and that the delay of each gate used in the negative level triggered latch is y units. The clock period may be assumed to be T.

- 1. Find the setup time, hold time, and the delays of the latches in terms of x and y.
 - The setup time of the positive level triggered latch is 3x and the hold time of the positive level triggered latch is 0.
 - The setup time of the negative level triggered latch is 2y and the hold time of the negative level triggered latch is y.
- 2. For what values of x and y will the master-slave D flip-flop function correctly? In particular, what is the smallest clock period (in terms of x and y) at which the D flip-flop will function correctly?
 - For correct operation, the following constraint must be met:

$$d_{D\to Q,B} + (S_A - S_B) \le T/2$$

The delay of the negative level triggered latch is 4y. Thus, we must have

$$4y + (3x - 2y) < T/2$$

or
$$T \ge 6x + 4y$$
.

- 3. Find the setup time, hold time and delay of the D flip-flop in terms of x and y.
 - Assuming that the flip-flop functions correctly, the setup and hold times of the D-flipflop are 2y and y respectively. The delay of the flip-flop is between 3x and 3x + 2y, or 3x + 2y in the worst case.

Suppose x = y = 1. Assume that the clock to the positive level triggered flip-flop is delayed by an amount w relative to the clock to the negative level triggered flip-flop. The clock period may be assumed to be T = 10.

- 1. For what values of w will the flip-flop function correctly?
 - If the clock to the slave flip-flop is internally delayed by w units, then its setup time will decrease by w units and its hold time will increase by w units. Also, for the circuit to function correctly, we must have

$$d_{Clock \to Q,B} \ge H_A$$

That is

$$4 \ge w$$

- 2. Assuming that w is chosen so that the flip-flop functions correctly, find the setup time, hold time and clock-to-q delay of the master-slave flip-flop in terms of w.
 - The setup and hold times are determined by the master and these do not change. The clock-to-q delay will increase by w, that is, it will be 5 + w.