


## EE 204-2018-2: Analog Circuits

### Homework #0 Solution

#### Question 1:

Solution- Homework #0

Ques 1

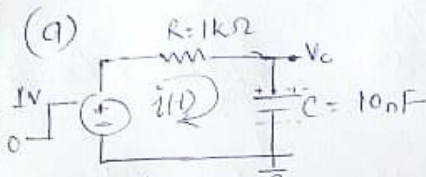

$$t \geq 0^+ \\ 1 - iR - V_c = 0 \quad \text{--- (1)}$$

differentiating the eqn (1)

$$-\frac{di}{dt}R - \frac{dV_c}{dt} = 0 \quad \text{--- (2)}$$

$$i = C \frac{dV_c}{dt} \quad \text{--- (3)}$$

from (2) and (3)

$$-\frac{di}{dt}R - \frac{i}{C} = 0$$

$$\frac{di}{dt} + \frac{i}{RC} = 0$$

solving the differential eqn.

$$i(t) = A e^{-\frac{t}{RC}} \quad \text{--- (4)}$$

at  $t = 0^+$  Capacitor acts as short ckt, hence  $i(0^+) = \frac{V}{R}$


$$i(0^+) = \frac{1}{1000} = 1\text{mA}$$

applying initial condition to eqn (4)

$$i(0^+) = A e^0 = 1\text{mA}$$

$$\Rightarrow A = 1\text{mA}$$
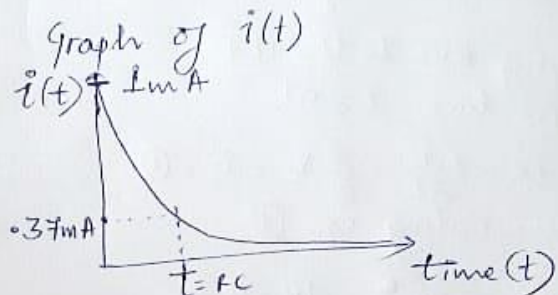
$$i(t) = 1\text{mA} e^{-\frac{t}{10 \times 10^{-6}}}$$



Here  $T = \text{time constant} = RC$

$$RC = 10 \times 10^{-9} \times 1000 \\ = 10\mu\text{s}$$


$$i(10\mu\text{s}) = 1\text{mA} e^{-\frac{10\mu\text{s}}{10\mu\text{s}}}$$

$$= 1\text{mA} e^{-1}$$

$$= 0.367$$

$$\Rightarrow 0.37\text{mA}$$

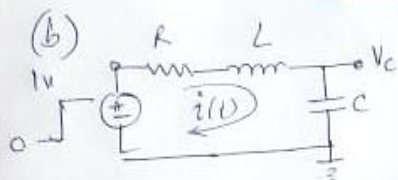Hence current is reduced by 67% in one time constant.



applying KVL to the ckt  
for time  $t \geq 0^+$

$$1 - iR - L \frac{di}{dt} - \frac{1}{C} \int i dt = 0 \quad (1)$$

differentiating eqn (1)

$$-R \frac{di}{dt} - L \frac{d^2 i}{dt^2} - \frac{1}{C} i = 0 \quad (2)$$

$$i = C \frac{dV_C}{dt} \quad (3)$$

from (3) and (4)

$$-R \frac{di}{dt} - L \frac{d^2 i}{dt^2} - \frac{i}{C} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \quad (5)$$

roots of above diff. eqn

$$= \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$= -0.9 \times 10^6, -0.1 \times 10^6$$

$$i(t) = A e^{-0.9 \times 10^6 t} + B e^{-0.1 \times 10^6 t} + C$$

at  $t = 0^+$   $i = 0 \Rightarrow A + B + C = 0$   
 $t = \infty$   $i = 0 \Rightarrow C = 0$

$$i(t) = A [e^{-0.9 \times 10^6 t} - e^{-0.1 \times 10^6 t}] \quad (6)$$

finding the value of A.

$$i = C \frac{dV_C}{dt}$$

$$\int_{-\infty}^t i dt = \int_0^t \frac{1}{C} \frac{dV_C}{dt} dt \quad (\text{H.K.D.})$$

$$V_C = \frac{1}{C} \int_{-\infty}^t i dt = \frac{1}{C} \int_0^t i dt \quad \left( \begin{array}{l} \text{because} \\ i = 0 \text{ for } t < 0 \end{array} \right)$$

$$= \frac{A}{C} \int_0^t (e^{-0.9 \times 10^6 t} - e^{-0.1 \times 10^6 t}) dt$$

$$V_C(t) = \frac{A}{C} \left[ \frac{e^{-0.9 \times 10^6 t}}{-0.9 \times 10^6} + \frac{e^{-0.1 \times 10^6 t}}{0.1 \times 10^6} \right]_0^t$$


at  $t = \infty$   $V_C(\infty) = 1V$

$$V_C(\infty) = \frac{A}{C} \left[ 0 - \left( -\frac{1}{0.9 \times 10^6} + \frac{1}{0.1 \times 10^6} \right) \right] = 1$$

$$A = -1.25 \times 10^{-3} \quad (7)$$

putting the value of A in eqn (6)


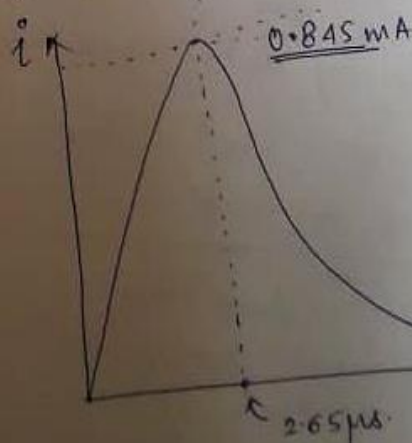
$$i(t) = -1.25 m (e^{-0.9 \times 10^6 t} - e^{-0.1 \times 10^6 t})$$



To find the value at which current is max. We need to find  $\frac{di}{dt} = 0$  (to calculate maxima)

at  $t = 2.65 \mu s$  the current is maximum.

$$i_{\max} \approx 0.845 \text{ mA}$$

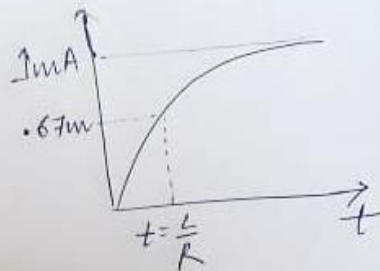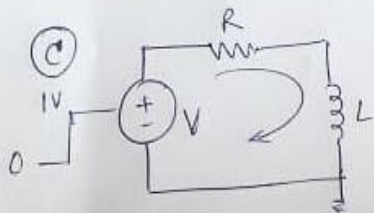

applying KVL for the time  $t \geq 0^+$

$$1 - iR - L \frac{di}{dt} = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{1}{L}$$

$$i(t) = A e^{-\frac{R}{L}t} + B$$

at  $t = 0^+$  inductor is open  
 $\Rightarrow i = 0$

$$\Rightarrow 0 = A + B$$


$$i(t) = A \left( e^{-\frac{R}{L}t} - 1 \right)$$

at  $t = \infty$ , inductor is short.

$$i(\infty) = \frac{1}{1k} = 1 \text{ mA}$$

$$1 \text{ m} = -A$$
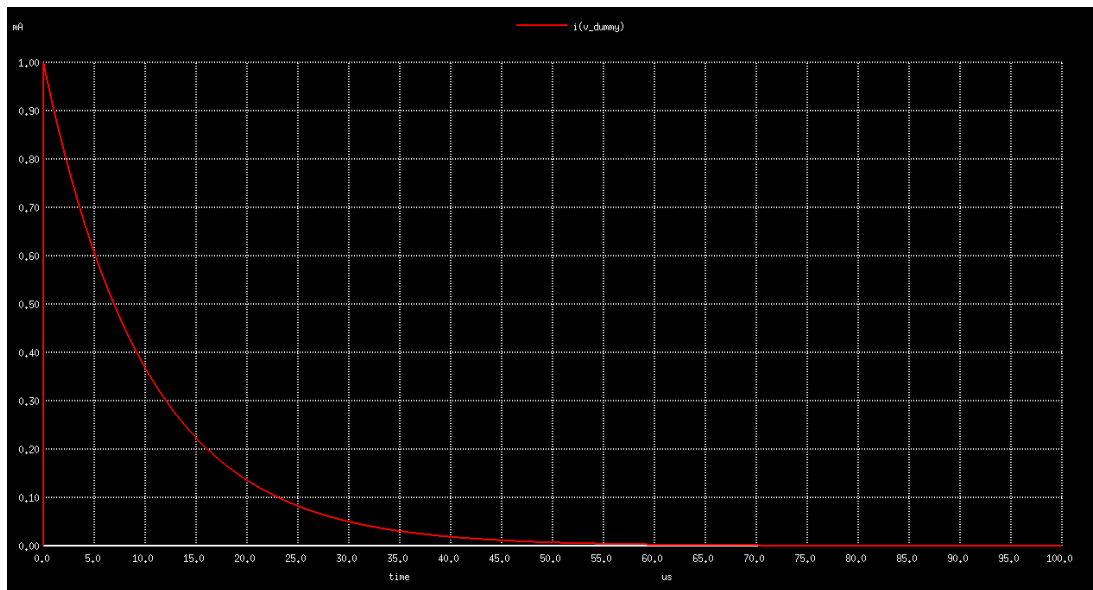
$$i(t) = 1 \text{ m} \left( 1 - e^{-\frac{R}{L}t} \right)$$



### SPICE Code Q1 (a):

\* Voltage Source

v1 1 gnd dc 1V

\* Dummy Voltage Source

v\_dummy 1 a 0V

\* Resistor

r1 a b 1k

\* Capacitor

c1 b gnd 10n ic=0V

.control

run


\* Transient Analysis [ tran <Step\_Size> <Stop\_Time> {<Start\_Time>} ]

tran 2n 100u uic

plot i(v\_dummy)

.endc

.end

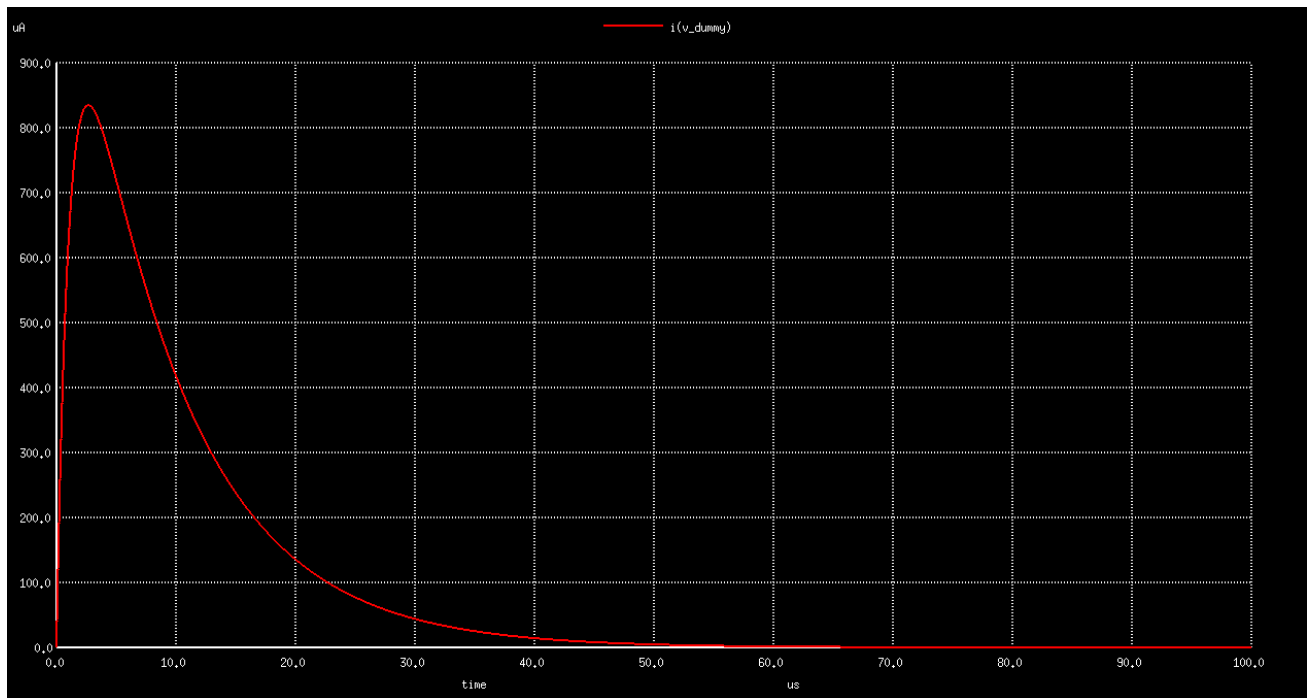

## SPICE Code Q1 (b)

\* Voltage Source

v1 1 gnd dc 1V

\* Dummy Voltage Source

v\_dummy 1 a 0V

\* Resistor

r1 a b 1k

\* Inductor

l1 b l\_end 1m ic=0A

\* Capacitor

c1 l\_end gnd 10n ic=0V

.control


\* Transient Analysis [ tran <Step\_Size> <Stop\_Time> {<Start\_Time>} ]

tran 2n 100u uic

plot i(v\_dummy)

.endc

.end

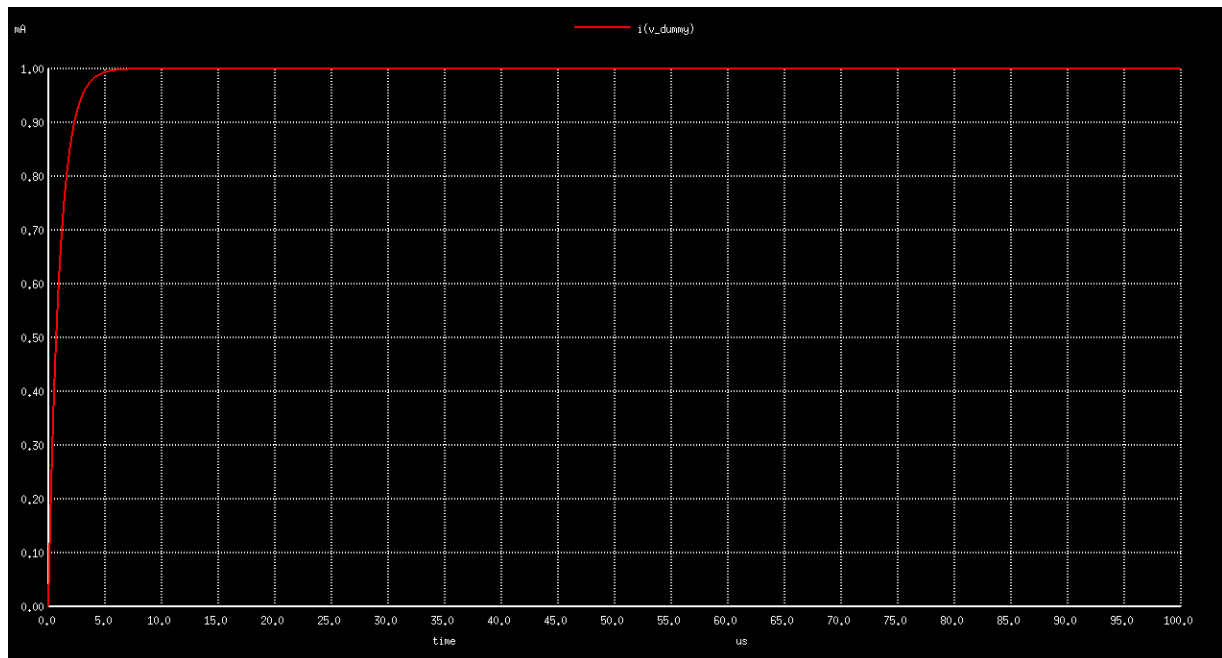

## SPICE Code Q1 (c)

\* Voltage Source

```
v1 1 gnd dc 1V
```

\* Dummy Voltage Source

```
v_dummy 1 a 0V
```

\* Resistor

```
r1 a b 1k
```

\* Inductor

```
l1 b gnd 1m ic=0A
```

```
.control
```

```
run
```

\* Transient Analysis [ tran <Step\_Size> <Stop\_Time> { <Start\_Time> } ]

```
tran 2n 100u uic
```

```
plot i(v_dummy)
```

```
.endc
```

```
.end
```




## Question 2:

### homework 0

②

①

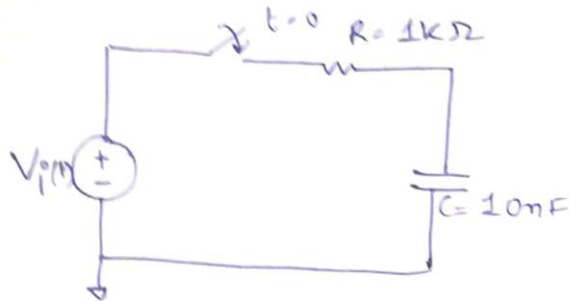

- $V_i(t) = \sin(2\pi \times 10^5 t + \pi/2)$

$$\Rightarrow V = 1 \angle 90^\circ$$

- $R = 1k\Omega$

$$\Rightarrow X_R = 10^3 \angle 0^\circ$$


- $C = 10nF$

$$\Rightarrow X_C = \frac{1 \angle -90^\circ}{\omega C} = \frac{1 \angle -90^\circ}{2\pi \times 10^5 \times 10 \times 10^{-9}} = \frac{10^3}{2\pi} \angle -90^\circ$$

$$I = \frac{V}{X_R + X_C} = \frac{1 \angle 90^\circ}{10^3 + \frac{10^3}{2\pi} \angle -90^\circ} = 9.875 \times 10^{-4} \angle 99.043^\circ$$

$$I_i(t) = 9.875 \times 10^{-4} \sin(2\pi \times 10^5 t + 0.55\pi)$$

⑥

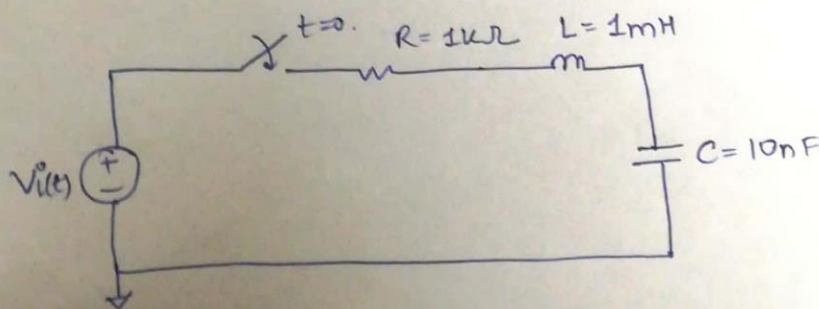

- $V = 1 \angle 90^\circ$

- $X_R = 10^3 \angle 0^\circ$

- $X_C = \frac{10^3}{2\pi} \angle -90^\circ$


- $L = 1mH \Rightarrow X_L = \omega L \angle 90^\circ = 2\pi \times 10^5 \times 10^{-3} \angle 90^\circ = 2\pi \times 10^2 \angle 90^\circ$

} from part ①

$$I = \frac{V}{X_R + X_L + X_C}$$

$$I = \frac{1 \angle 90^\circ}{10^3 + \cancel{2\pi \times 10^2} \angle 90^\circ + \frac{10^3}{2\pi} \angle -90^\circ} = 9.053 \times 10^{-4} \angle 64.865$$
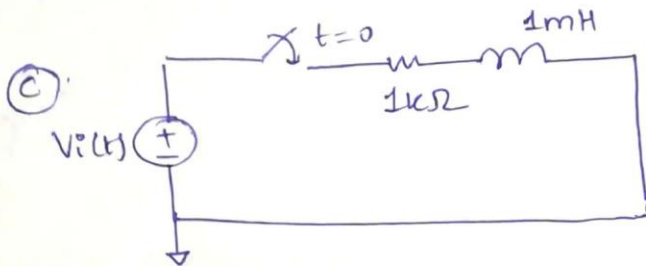
$$I_i(t) = 9.053 \times 10^{-4} \sin(2\pi \times 10^5 t + 0.36\pi)$$



- $V = 1 \angle 90^\circ$
  - $X_R = 10^3$
  - $X_L = 2\pi \times 10^2 \angle 90^\circ$
- } from ① and ②


$$I = \frac{V}{X_R + X_L} = \frac{1 \angle 90^\circ}{10^3 + 2\pi \times 10^2 \angle 90^\circ} = 8.467 \times 10^{-4} \angle 57.858$$

$$I_i(t) = 8.467 \times 10^{-4} \sin(2\pi \times 10^5 t + 0.321\pi)$$




### Question 3:

3.

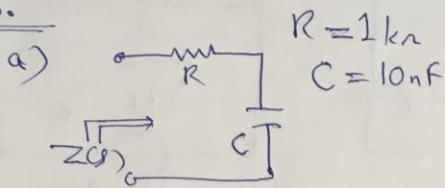


$$Z_a(s) = R + \frac{1}{sC}$$
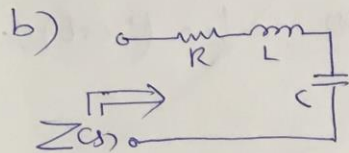
$$\therefore Z_a(j\omega) = R - j \cdot \left( \frac{1}{\omega C} \right) = 1000 - j \left( \frac{1}{10^{-8} \cdot \omega} \right)$$



$$Z_b(s) = R + sL + \frac{1}{sC}$$
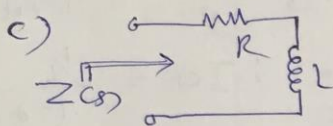
$$\therefore Z_b(j\omega) = R + j \left( \omega L - \frac{1}{\omega C} \right) = R + j \left( 10^{-3} - \frac{1}{10^{-8} \cdot \omega} \right)$$



$$Z_c(s) = R + sL$$

$$\therefore Z_c(j\omega) = R + j\omega L = 1000 + j(10^{-3}\omega)$$


Magnitude:

$$|Z_a(j\omega)| = \sqrt{1000^2 + \frac{1}{10^{-16}\omega^2}}$$

$$|Z_b(j\omega)| = \sqrt{1000^2 + \left( 10^{-3}\omega - \frac{1}{10^{-8}\omega} \right)^2}$$

$$|Z_c(j\omega)| = \sqrt{1000^2 + 10^{-6}\omega^2}$$

with  $\omega = 2\pi f \text{ rad/s}$

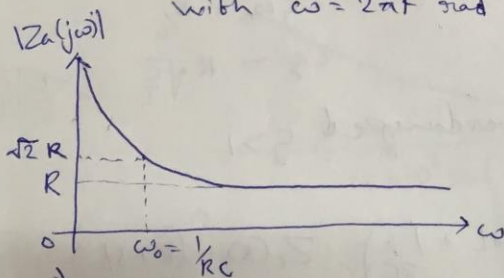



Phase:

$$\angle Z_a(j\omega) = \tan^{-1} \left( \frac{-1}{\omega RC} \right)$$

$$\angle Z_b(j\omega) = \tan^{-1} \left( \frac{\omega L - 1/\omega C}{R} \right)$$

$$\angle Z_c(j\omega) = \tan^{-1} \left( \frac{\omega L}{R} \right)$$


with  $\omega = 2\pi f \text{ rad/s}$

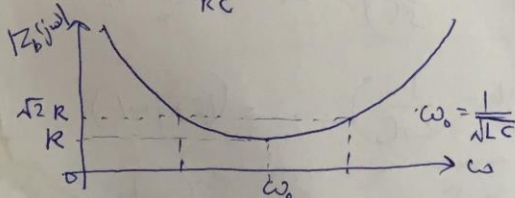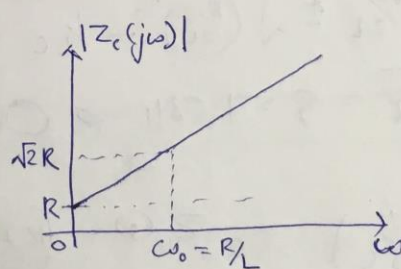

$$\omega_{0(a)} = 10^5 \text{ rad/s}$$


$$\omega_{0(c)} = 10^6 \text{ rad/s}$$
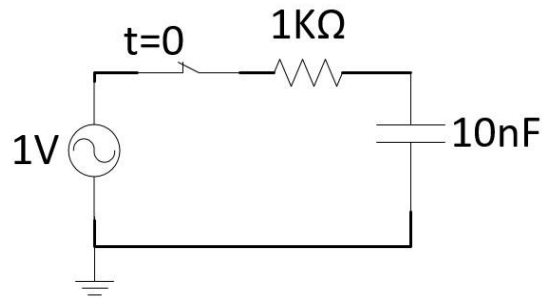
$$\omega_{0(b)} = 3.1623 \times 10^5 \text{ rad/s}$$




(a)

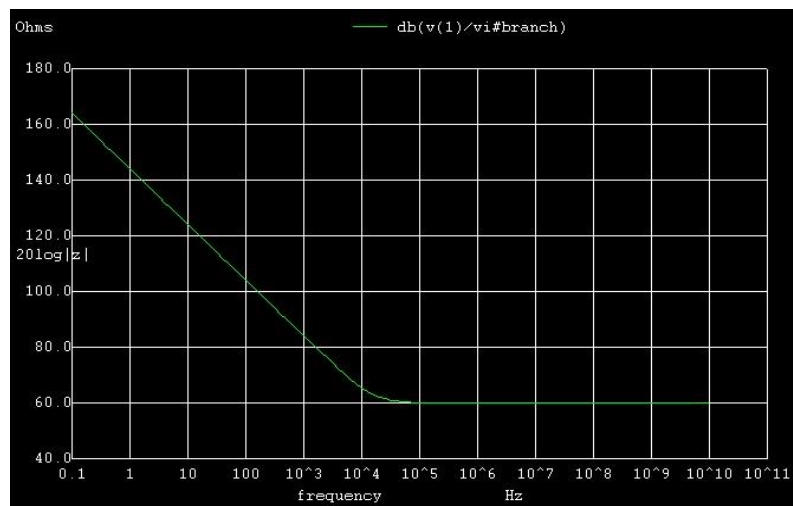
Impedance (Magnitude) as a function of frequency: log scale



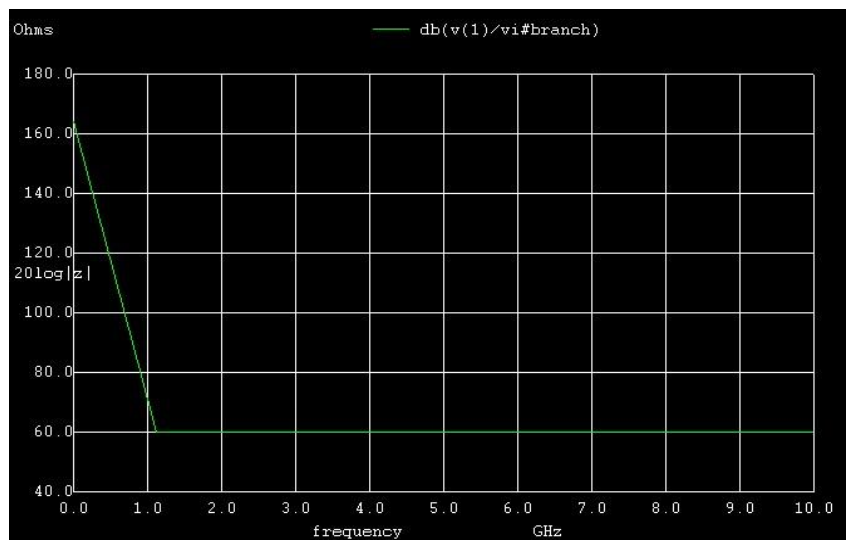
Impedance (Magnitude) as a function of frequency: linear scale



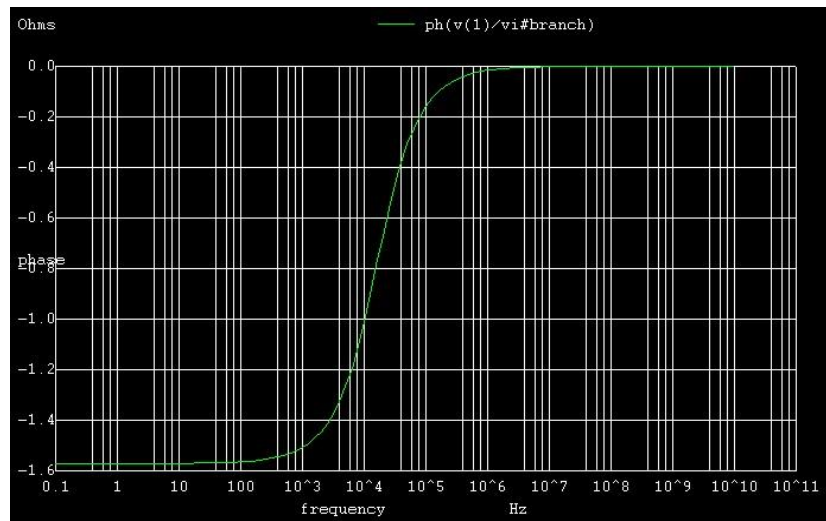Impedance (Phase) as a function of frequency: log scale



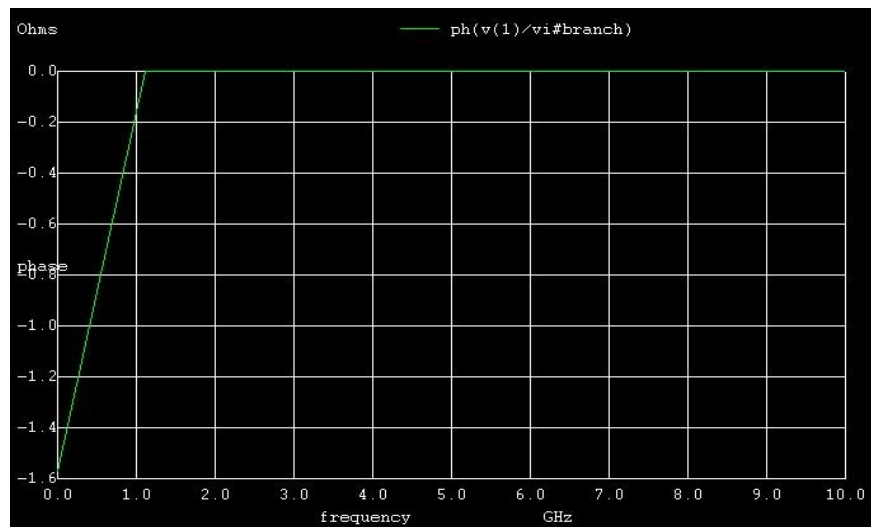Impedance (Phase) as a function of frequency: linear scale



### Spice code for RC circuit: Q3 (a)

\*input impedance of RC ckt - log scale

```
r1 1 2 1k
c1 2 0 10n
vi a 1 0
vin a 0 dc 0 ac 1
.ac dec 10 0.1 10g

.control
run

plot db(v(1)/vi#branch) xlabel frequency ylabel 20log|Z|
plot ph(v(1)/vi#branch) xlabel frequency ylabel Phase
.endc
.end
```


---

\*input impedance of RC ckt – linear scale

```
r1 1 2 1k
c1 2 0 10n
vi a 1 0
vin a 0 dc 0 ac 1
.ac lin 10 0.1 10g


.control
run

plot db(v(1)/vi#branch) xlabel frequency ylabel 20log|Z|
plot ph(v(1)/vi#branch) xlabel frequency ylabel Phase
.endc
.end
```

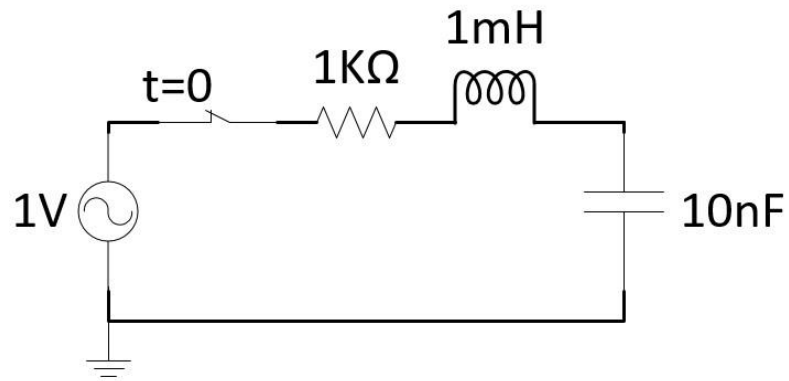


(b)

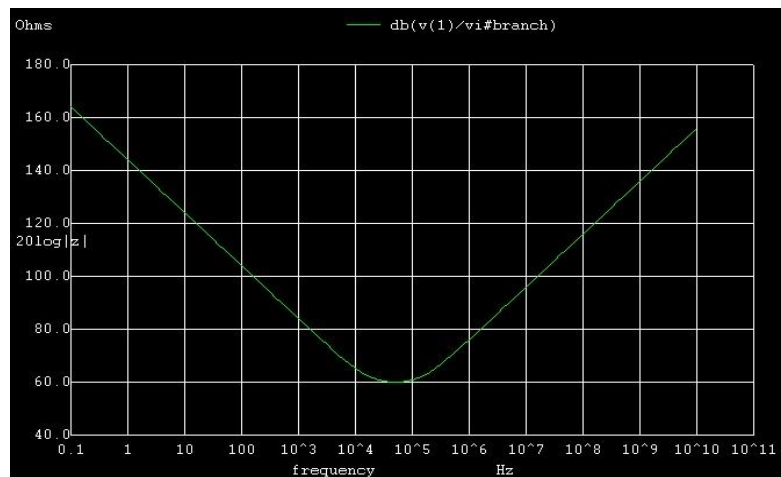Impedance (Magnitude) as a function of frequency: log scale




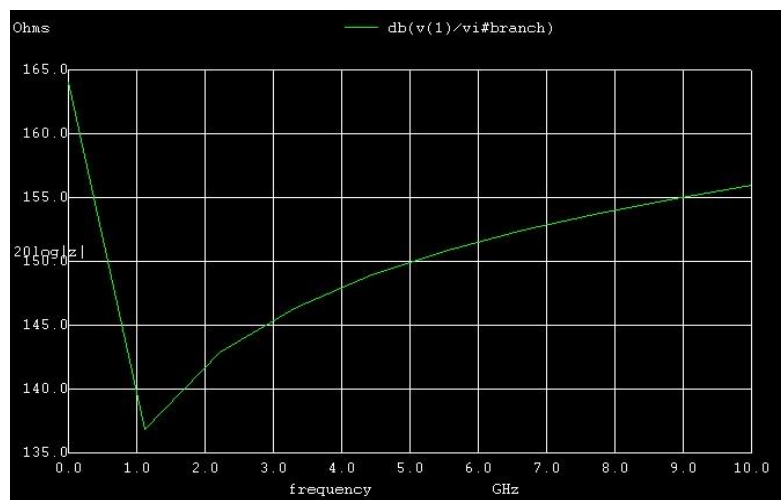Impedance (Magnitude) as a function of frequency: linear scale






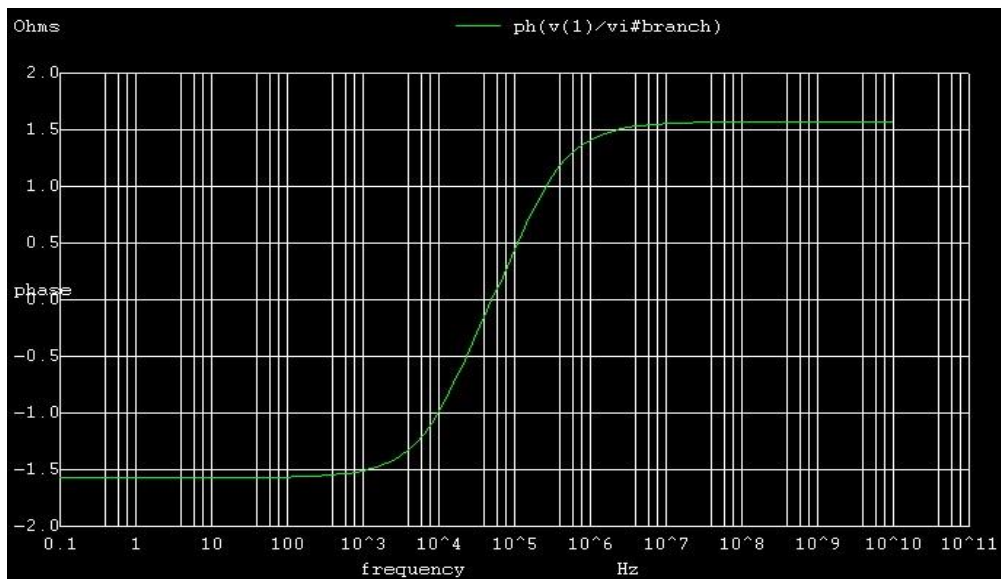Impedance (Phase) as a function of frequency: log scale



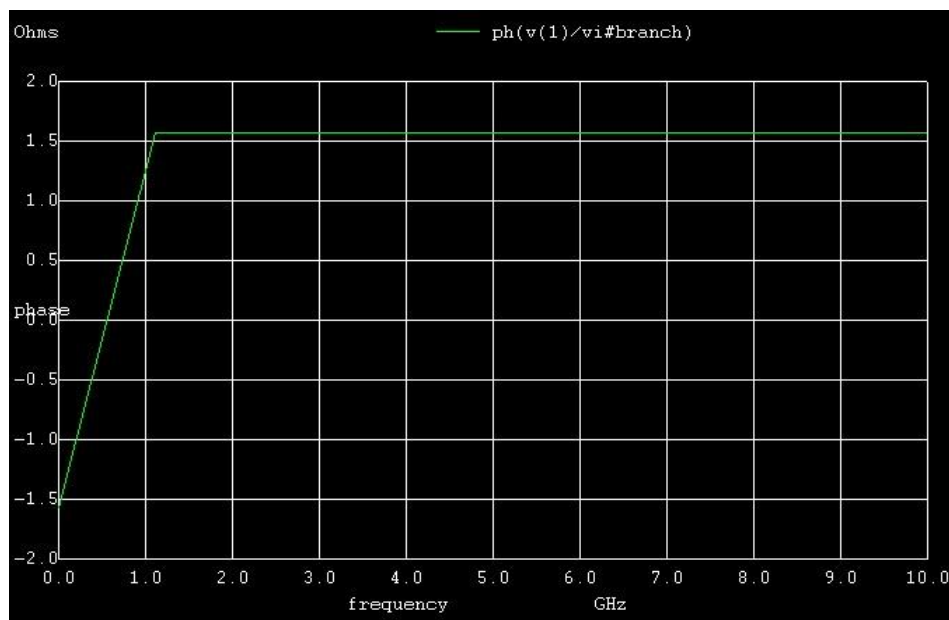Impedance (Phase) as a function of frequency: linear scale



### Spice code for RLC circuit: Q3 (b)

\*input impedance of RLC ckt – log scale

```
r1 1 2 1k
l1 2 3 1m
c1 3 0 10n
vi a 1 0
vin a 0 dc 0 ac 1
.ac dec 10 0.1 10g

.control
run

plot db(v(1)/vi#branch) xlabel frequency ylabel 20log|Z|
plot ph(v(1)/vi#branch) xlabel frequency ylabel Phase
.endc
.end
```


---

\*input impedance of RLC ckt – linear scale

```
r1 1 2 1k
l1 2 3 1m
c1 3 0 10n
vi a 1 0
vin a 0 dc 0 ac 1
.ac lin 10 0.1 10g


.control
run

plot db(v(1)/vi#branch) xlabel frequency ylabel 20log|Z|
plot ph(v(1)/vi#branch) xlabel frequency ylabel Phase
.endc
.end
```

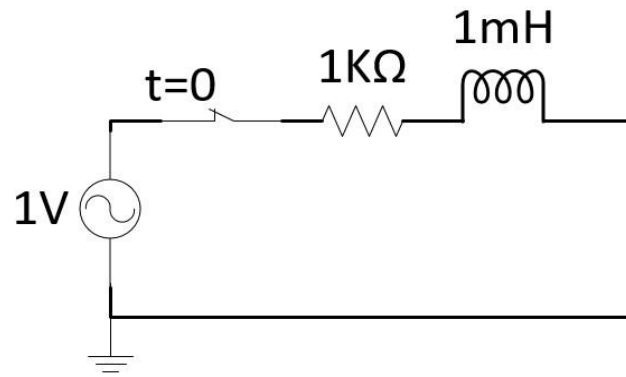


(c)

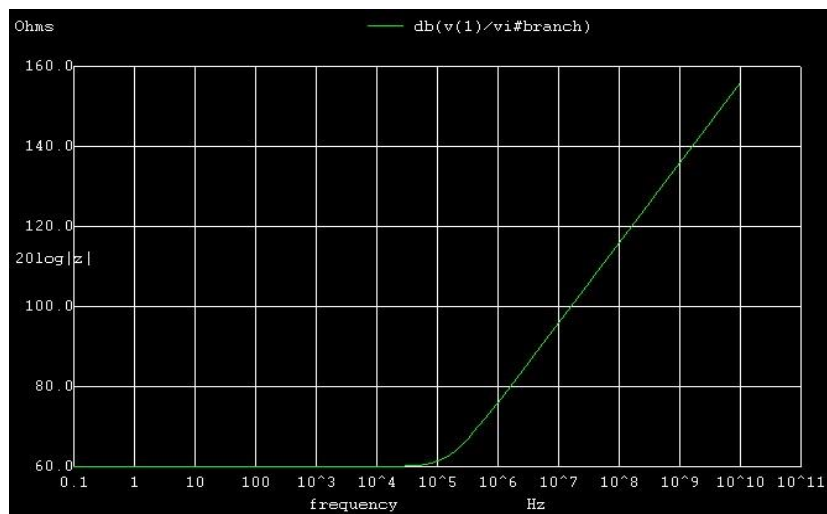
Impedance (Magnitude) as a function of frequency: log scale



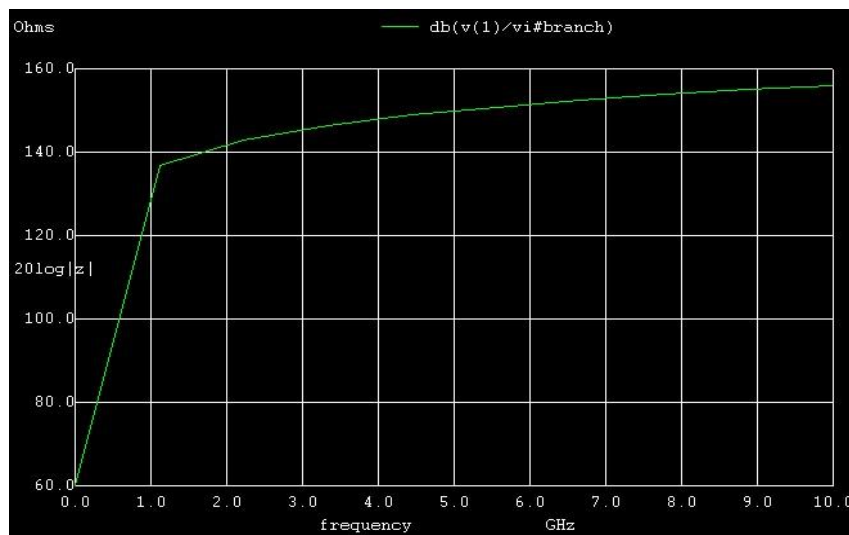
Impedance (Magnitude) as a function of frequency: linear scale



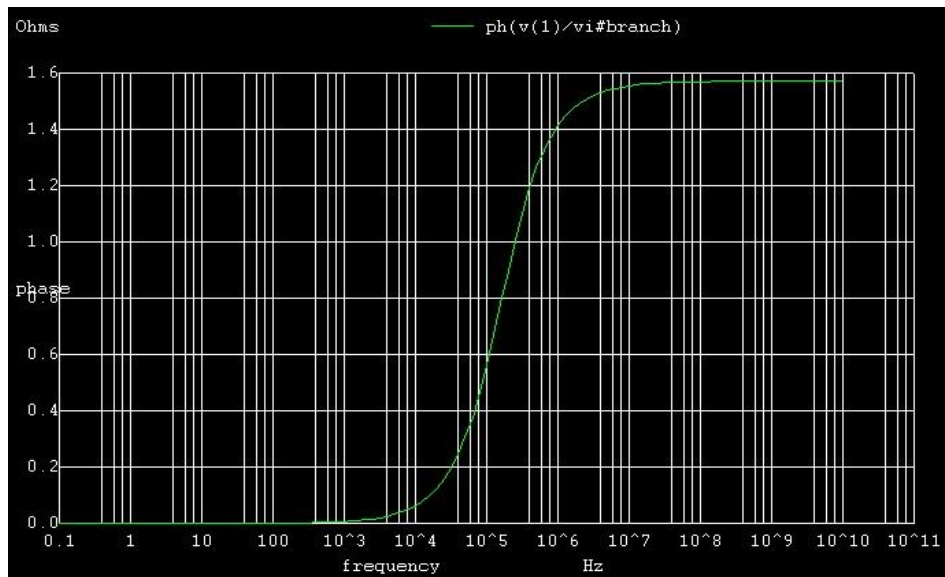Impedance (Phase) as a function of frequency: log scale



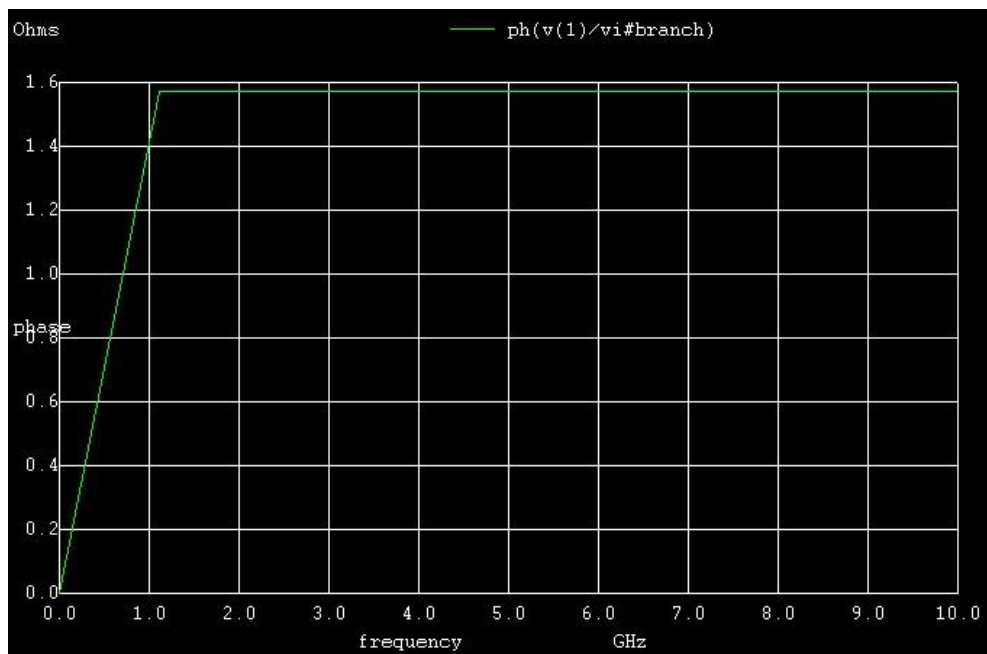Impedance (Phase) as a function of frequency: linear scale



### Spice code for RL circuit: Q3 (c)

\*input impedance of RL ckt – log scale

```
r1 1 2 1k
l1 2 0 1m
vi a 1 0
vin a 0 dc 0 ac 1
.ac dec 10 0.1 10g

.control
run

plot db(v(1)/vi#branch) xlabel frequency ylabel 20log|Z|
plot ph(v(1)/vi#branch) xlabel frequency ylabel Phase
.endc
.end
```

---

\*input impedance of RL ckt – linear scale

```
r1 1 2 1k
l1 2 0 1m
vi a 1 0
vin a 0 dc 0 ac 1
.ac lin 10 0.1 10g

.control
run

plot db(v(1)/vi#branch) xlabel frequency ylabel 20log|Z|
plot ph(v(1)/vi#branch) xlabel frequency ylabel Phase
.endc
.end
```