

EE224: End-semester Test

24 April 2014, 1730-2030 hrs

All questions have 5 marks. Make suitable assumptions if needed, and mention them clearly.

1. Suppose $f(x_1, x_2, x_3, x_4)$ is a function of four variables. Derive a procedure to check if it is possible to factorize

$$f(x_1, x_2, x_3, x_4) = g(x_1, x_2).h(x_3, x_4)$$

where g and h are functions of two variables (5 marks). Apply your procedure to find suitable factors g, h (or show that no such factors exist) if

$$f(x_1, x_2, x_3, x_4) = x_1.(x_4.x_2.\bar{x}_3 + x_3.\bar{x}_4.x_2) + \bar{x}_1.(\bar{x}_3.\bar{x}_2.\bar{x}_4 + \bar{x}_2.\bar{x}_3.x_4).$$

2. Consider the two state-machines shown in Figure 1. The left-machine has states $\{S0, S1\}$, input symbols $\{rL, f, s\}$ and output symbols $\{rR, u, v\}$. The right-machine has states $\{T0, T1\}$, input symbols $\{rR, u, v\}$ and output symbols $\{d, n\}$. The output of the left-machine is the input to the right-machine. Taken together, the pair of state machines is equivalent to a single FSM with four states, input symbols $\{rL, u, v\}$ and output symbols $\{d, n\}$. Draw the state-transition graph of this equivalent FSM.
3. Using two input NAND gates, inverters and D-flipflops, implement the state machine shown in Figure 2. The input symbols are $\{S, C, T, N\}$, the output symbols are $\{H, L\}$ and the states are $\{Q0, Q1\}$. Clearly show your input, output and state encodings and any intermediate work you do in getting to your implementation. Assume that all gates have unit delay, and the D-flipflop has delay, setup and hold times which are all equal to 1 unit. For your solution, find the

 


Figure 1: Interacting FSMs

 


Figure 2: FSM specification

- input setup times relative to clock (for each input).
 - input hold times relative to clock (for each input).
 - delay from clock to output.
4. Consider the circuit shown in Figure 3. The capacitances shown correspond to wire capacitances. The variables x, y, z are input capacitances of the three gates. For the circuit, it is required that $C_{in} = 1$ and $C_{out} = 4$ units. Write the total delay of the circuit as a function of x, y, z (in τ units). For what values of x, y, z is the minimum delay achieved (assume that x, y, z are positive real numbers)? What is the minimum delay?
 5. The pseudo-code in Figure 4 describes an 8-bit divider. Simulate the

 


Figure 3: Inverter Chain

pseudo code (calculate the state and register values at the different k instants) until the `div_done` output signal becomes 1. The system starts in `div_reset` at $k = 0$ and at $k = 1$, `div_start` is 1. The divisor input is maintained at 00011100 and the dividend input is maintained at 10101110 throughout the period of interest. Does it work?

6. Consider the VHDL description of a piece of logic.

```
-- a, b, c, d are bits.
process(a,b,c,d, clk)
    variable x,y: bit;
begin
    x := (a or b);
    if(b = '1') then
        x := (not x);
    else
        x := (x or c);
    end if;
    if(c = '1') then
        x := (x and d);
    end if;
    e <= x;
    y := (not (x and (a or b)));
    if(clk'event and clk = '1') then
        q <= y;
    end if;
end process;
```

Draw a logic network which is equivalent to this process statement

```

// divisor, dividend are 8-bit inputs.
// remainder, dividend_by_2 shifted_divisor,
// quotient are all 8-bits wide registers.
reset:
    if div_start then
        goto div_outerloop/
            {remainder = dividend || quotient = 0}
    else
        goto div_reset
    endif

div_outerloop:
    if (divisor <= remainder) then
        goto div_innerloop/
            { curr_quotient = "0000000000000001" ||
              dividend_by_2 = (remainder >> 1) ||
              shifted_divisor = divisor}
    else
        goto div_completed
    endif

div_innerloop:
    if (shifted_divisor < dividend_by_2) then
        goto div_innerloop/
            { shifted_divisor = (shifted_divisor << 1) ||
              curr_quotient = (curr_quotient << 1) }
    else
        goto div_update
    endif

div_update:
    goto div_outerloop/
        {quotient = (quotient OR curr_quotient) ||
         remainder = (remainder - shifted_divisor)}

div_completed:
    goto div_reset/{emit div_done}

```

Figure 4: Divider

(you may use AND, OR, NOT gates and D-flip-flops).

7. You are asked to design a system which receives a sequence of bits $\{x(k)\}$ and produces an output sequence of bits $\{y(k)\}$ such that $y(k) = 1$ if and only if the bits $x(0), x(1), \dots, x(k)$ form a palindrome (that is a sequence which reads the same from left to right as it does from right to left, for example 1, 1, 0, 1, 1). Can you implement such a system using a Mealy finite state machine? If yes, give the state transition graph of the FSM. If not, why not? (5 marks).
8. Suppose you are given a collection of combinational gates each of which is a four-input programmable logic block which can implement any four-input Boolean function. Using these gates, implement a majority voter function which has eight input bits and outputs a 1 if and only if least 5 of its input bits are 1 (5 marks).
9. Design a CMOS gate to implement the Boolean function $\overline{(A + B)} \cdot \overline{(C + D)}$ with a single size parameter W and size it so that the pull-up and pull-down networks are equivalent to a $2W$ PMOS transistor and W NMOS transistor respectively. What is the logical effort of the gate relative to that of a standard inverter?
10. Do you agree or disagree with the following statements? In each case, give a short justification for your opinion.
 - In a well designed CMOS circuit, all nodes should have approximately the same rise/fall times.
 - In a well designed CMOS circuit, all paths should have approximately the same delays.
 - In a well designed CMOS circuit, all gates should be minimum sized.
 - A digital system with many clocks is easier to implement and verify than one with a single clock.
 - When implementing a digital system, most of the time should be spent in VHDL/Verilog coding.